
LECTURE 39 – OVERSAMPLING ADCS – PART I

LECTURE ORGANIZATION

Outline

- Introduction
- Delta-sigma modulators
- Summary

CMOS Analog Circuit Design, 3rd Edition Reference

Pages 589-596

INTRODUCTION

What is an oversampling converter?

An oversampling converter uses a noise-shaping modulator to reduce the in-band quantization noise to achieve a high degree of resolution.

- What is the range of oversampling?

The oversampling ratio, called M , is a ratio of the sampling frequency to the Nyquist frequency of the input signal. The Nyquist frequency is twice the bandwidth of the input signal. This oversampling ratio can vary from 8 to 256.

- The resolution of the oversampled converter is proportional to the oversampled ratio.
- The bandwidth of the input signal is inversely proportional to the oversampled ratio.

- What are the advantages of oversampling converters?

Very compatible with VLSI technology because most of the converter is digital
High resolution

Single-bit quantizers use a one-bit DAC which has no INL or DNL errors

Provide an excellent means of trading precision for speed (16-18 bits with a signal bandwidth of 50kHz to 8-10 bits with a signal bandwidth of 5-10MHz).

- What are the disadvantages of oversampling converters?

Difficult to model and simulate

Limited in bandwidth to the clock frequency divided by the oversampling ratio

Nyquist Versus Oversampled ADCs

Conventional Nyquist ADC Block Diagram:

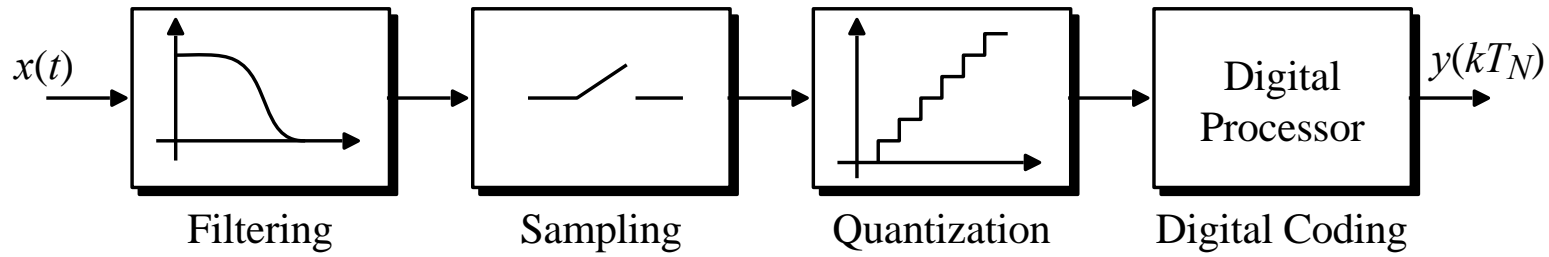


Fig.10.9-01

Oversampled ADC Block Diagram:

 


Fig.10.9-02

Components:

- Filter - Prevents possible aliasing of the following sampling step.
- Sampling - Necessary for any analog-to-digital conversion.
- Quantization - Decides the nearest analog voltage to the sampled voltage (determines the resolution).
- Digital Coding - Converts the quantizer information into a digital output signal.

Frequency Spectrum of Nyquist and Oversampled Converters

Definitions:

f_B = analog signal bandwidth


f_N = Nyquist frequency (two times f_B)

f_S = sampling or clock frequency

$M = \frac{f_S}{f_N} = \frac{f_S}{2f_B}$ = oversampling ratio

Frequency prespective:

 Conventional ADC with $f_B \approx 0.5f_N = 0.5f_S$.



Oversampled ADC with $f_B \approx 0.5f_N \ll f_S$.

 


Fig.10.9-03

Quantization Noise of a Conventional (Nyquist) ADC

Multilevel Quantizer:

The quantized signal y can be represented as,

$$y = Gx + e$$


where

G = gain of the ADC, normally 1

e = quantization error

The mean square value of the quantization error is
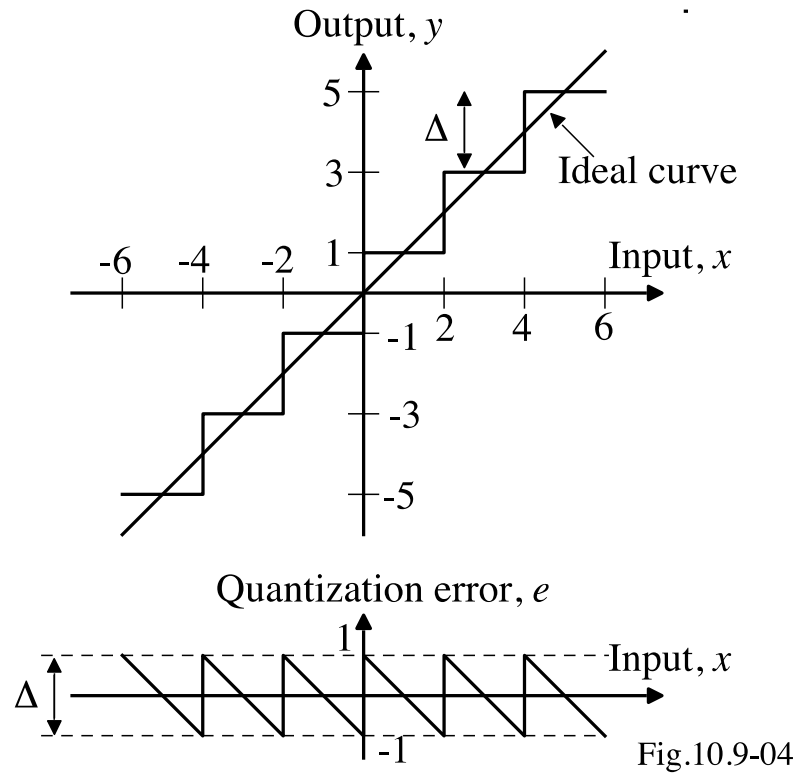
$$e_{rms}^2 = S_Q = \frac{1}{\Delta} \int_{-\Delta/2}^{\Delta/2} e(x)^2 dx = \frac{\Delta^2}{12}$$



Quantization Noise of a Conventional (Nyquist) ADC - Continued

Spectral density of the sampled noise:

When a quantized signal is sampled at $f_S (= 1/\tau)$, then all of its noise power folds into the frequency band from 0 to $0.5f_S$. Assuming that the noise power is white, the spectral density of the sampled noise is,

$$E(f) = e_{rms} \sqrt{\frac{2}{f_S}} = e_{rms} \sqrt{2\tau}$$

where $\tau = 1/f_S$ and $f_S =$ sampling frequency. The inband noise energy n_o is

$$n_o^2 = \int_0^{f_B} E^2(f) df = e_{rms}^2 (2f_B \tau) = e_{rms}^2 \left(\frac{2f_B}{f_S} \right) = \frac{e_{rms}^2}{M} \quad \Rightarrow \quad n_o = \frac{e_{rms}}{\sqrt{M}}$$

What does all this mean?


- One way to increase the resolution of an ADC is to make the bandwidth of the signal, f_B , less than the clock frequency, f_S . In other words, give up bandwidth for precision.
- However, it is seen from the above that a doubling of the oversampling ratio M , only gives a decrease of the inband noise, n_o , of $1/\sqrt{2}$ which corresponds to -3dB decrease or an increase of resolution of 0.5 bits.

As a result, increasing the oversampling ratio of a Nyquist analog-digital converter is not a very good method of increasing the resolution.

Oversampled Analog-Digital Converters


Classification of oversampled ADCs:

 1.) Straight-oversampling - The quantization noise is assumed to be equally distributed over the entire frequency range of dc to $0.5f_s$. This type of converter is represented by the Nyquist ADC.



2.) Predictive oversampling - Uses noise shaping plus oversampling to reduce the inband noise to a much greater extent than the straight-oversampling ADC. Both the signal and noise quantization spectrums are shaped.

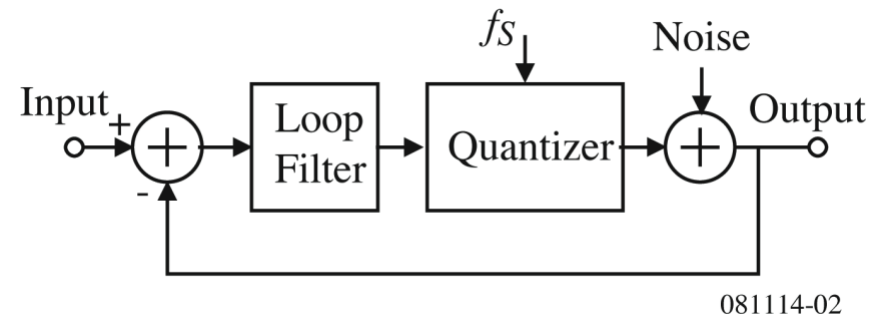3.) Noise-shaping oversampling - Similar to the predictive oversampling except that only the noise quantization spectrum is shaped while the signal spectrum is preserved.



The noise-shaping oversampling ADCs are also known as *delta-sigma* ADCs. We will only consider the delta-sigma type oversampling ADCs.

DELTA-SIGMA MODULATORS

General block diagram of an oversampled ADC

Components of the Oversampled ADC:

 


Fig.10.9-07

- 1.) $\Delta\Sigma$ Modulator - Also called the noise shaper because it can shape the quantization noise and push the majority of the inband noise to higher frequencies. It modulates the analog input signal to a simple digital code, normally a one-bit serial stream using a sampling rate much higher than the Nyquist rate.
- 2.) Decimator - Also called the down-sampler because it down samples the high frequency modulator output into a low frequency output and does some pre-filtering on the quantization noise.
- 3.) Digital Lowpass Filter - Used to remove the high frequency quantization noise and to preserve the input signal.

Note: Only the modulator is analog, the rest of the circuitry is digital.

First-Order, Delta-Sigma Modulator

Block diagram of a first-order, delta-sigma modulator:

Components:

- Integrator (continuous or discrete time)
- Coarse quantizer (typically two levels)
 - A/D which is a comparator for two levels
 - D/A which is a switch for two levels

First-order modulator output for a sinusoidal input:

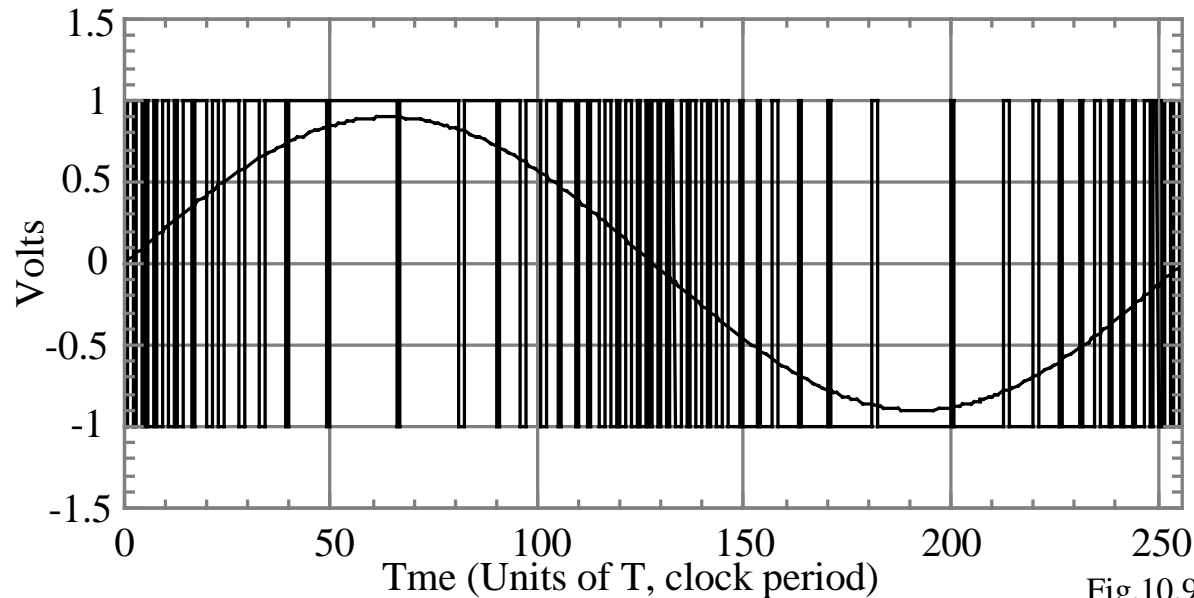


Fig.10.9-09

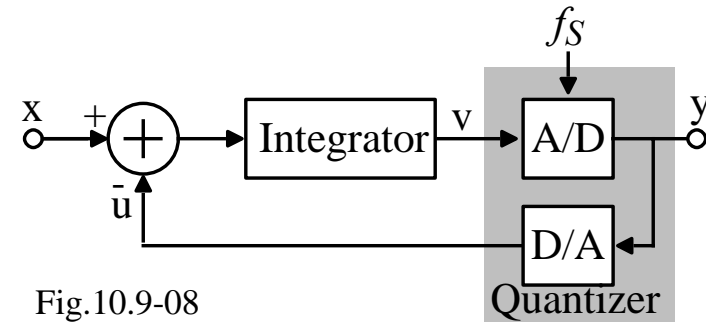


Fig.10.9-08

Sampled-Data Model of a First-Order $\Delta\Sigma$ Modulator

Writing the following relationships,

$$y[nT_s] = q[nT_s] + v[nT_s]$$

$$v[nT_s] = w[(n-1)T_s] + v[(n-1)T_s]$$

 


Fig. 10.9-10

$$\therefore y[nT_s] = q[nT_s] + w[(n-1)T_s] + v[(n-1)T_s] = q[nT_s] + \{x[(n-1)T_s] - y[(n-1)T_s]\} + v[(n-1)T_s]$$

But the first equation can be written as

$$y[(n-1)T_s] = q[(n-1)T_s] + v[(n-1)T_s] \quad \rightarrow \quad q[(n-1)T_s] = y[(n-1)T_s] - v[(n-1)T_s]$$

Substituting this relationship into the above gives,

$$y[nT_s] = x[(n-1)T_s] + q[nT_s] - q[(n-1)T_s]$$

Converting this expression to the z -domain gives,

$$Y(z) = z^{-1}X(z) + (1-z^{-1})Q(z)$$


Definitions:

$$\text{Signal Transfer Function} = STF = \frac{Y(z)}{X(z)} = z^{-1}$$

$$\text{Noise Transfer Function} = NTF = \frac{Y(z)}{Q(z)} = 1-z^{-1}$$

Higher-Order $\Delta\Sigma$ Modulators

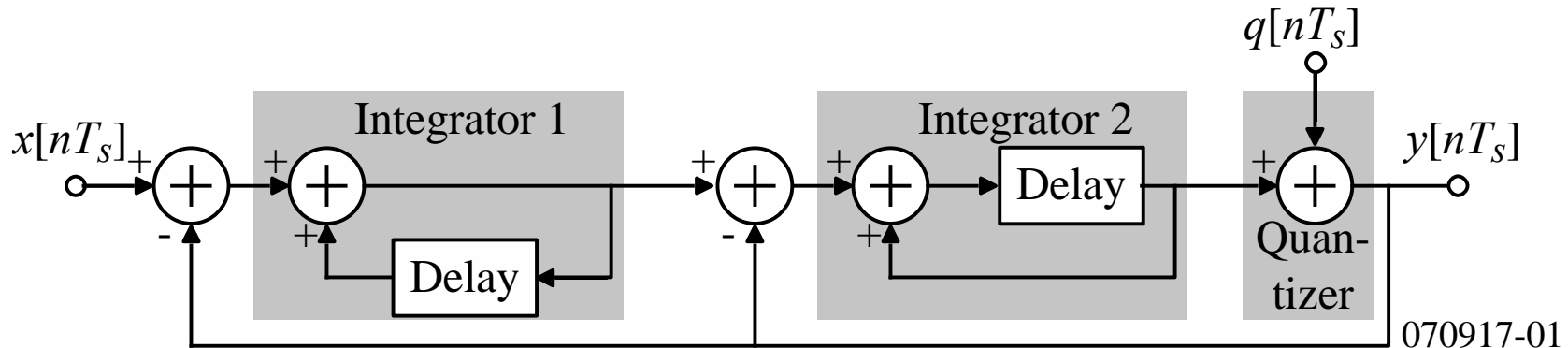A second-order, $\Delta\Sigma$ modulator:



It can be shown that the z -domain output is,

$$Y(z) = z^{-1}X(z) + (1-z^{-1})^2Q(z)$$

The general, L -th order $\Delta\Sigma$ modulator has the following form,

$$Y(z) = z^{-K}X(z) + (1-z^{-1})^LQ(z)$$

Note that noise transfer function, NTF , has L -zeros at the origin resulting in a high-pass transfer function. K depends on the architecture where $K \leq L$.

This high-pass characteristic reduces the noise at low frequencies which is the key to extending the dynamic range within the bandwidth of the converter.

Noise Transfer Function

The noise transfer function can be written as,

$$NTF_Q(z) = (1-z^{-1})^L$$

Evaluate $(1-z^{-1})$ by replacing z by $e^{j\omega T_s}$ to get

$$(1-z^{-1}) = (1 - e^{-j\omega T_s}) \left(\frac{2j}{2j} \right) \frac{e^{j\pi f/f_s}}{e^{j\pi f/f_s}} = \left(\frac{e^{j\pi f/f_s} - e^{-j\pi f/f_s}}{2j} \right) 2j e^{-j\pi f/f_s} = \sin(\pi f T_s) 2j e^{-j\pi f/f_s}$$

$$|1-z^{-1}| = (2\sin\pi f T_s) \quad \rightarrow \quad |NTF_Q(f)| = (2\sin\pi f T_s)^L$$

Magnitude of the noise transfer function,

Note: Single-loop modulators having noise shaping characteristics of the form $(1-z^{-1})^L$ are unstable for $L > 2$ unless an L -bit quantizer is used.

 


Fig.10.9-12

In-Band Rms Noise of Single-Loop $\Delta\Sigma$ Modulator

Assuming noise power is white, the power spectral density of the $\Delta\Sigma$ modulator, $S_E(f)$, is

$$S_E(f) = |NTF_Q(f)|^2 \frac{|S_Q(f)|}{f_s}$$

Next, integrate $S_E(f)$ over the signal band to get the inband noise power using $S_Q = \frac{\Delta^2}{12}$

$$\therefore S_B = \frac{1}{f_s} \int_{-f_b}^{f_b} (2 \sin \pi f T_s)^{2L} \frac{\Delta^2}{12} df \approx \left(\frac{\pi^{2L}}{2L+1} \right) \left(\frac{1}{M^{2L+1}} \right) \left(\frac{\Delta^2}{12} \right) \quad \text{where } \sin \pi f T_s \approx \pi f T_s \text{ for } M \gg 1.$$

Therefore, the in-band, rms noise is given as

$$n_0 = \sqrt{S_B} = \left(\frac{\pi^L}{\sqrt{2L+1}} \right) \left(\frac{1}{M^{L+0.5}} \right) \left(\frac{\Delta}{\sqrt{12}} \right) = \left(\frac{\pi^L}{\sqrt{2L+1}} \right) \left(\frac{1}{M^{L+0.5}} \right) e_{rms}$$

Note that the $\Delta\Sigma$ is a much more efficient way of achieving resolution by increasing M .

$$n_0 \propto \frac{e_{rms}}{M^{L+0.5}} \Rightarrow \text{Doubling of } M \text{ leads to a } 2^{L+0.5} \text{ decrease of in-band noise}$$


resulting in an extra $L+0.5$ bits of resolution!

\therefore The increase of the oversampling ratio is an excellent method of increasing the resolution of a $\Delta\Sigma$ oversampling analog-digital converter.

Illustration of RMS Noise Versus Oversampling Ratio for Single Loop $\Delta\Sigma$ Modulators

Plotting n_0/e_{rms} gives,
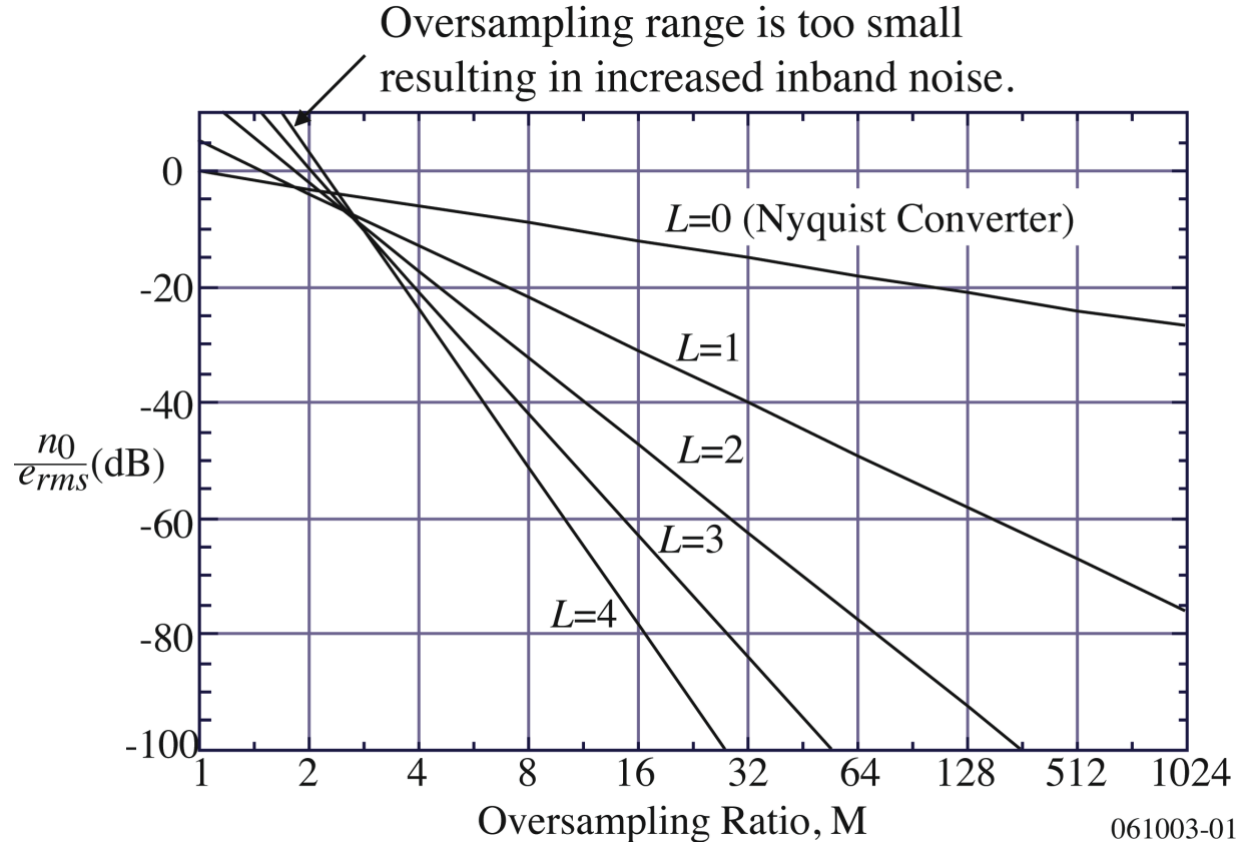
$$\frac{n_0}{e_{rms}} = \left(\frac{\pi L}{\sqrt{2L+1}} \right) \left(\frac{1}{M^{L+0.5}} \right)$$



Dynamic Range of $\Delta\Sigma$ Analog-Digital Converters

Oversampled $\Delta\Sigma$ Converter:

The dynamic range, DR , for a 1 bit-quantizer with level spacing $\Delta = V_{REF}$, is

$$DR^2 = \frac{\text{Maximum signal power}}{S_B(f)} = \frac{\left(\frac{\Delta}{2\sqrt{2}}\right)^2}{\left(\frac{\pi^2 L}{2L+1}\right)\left(\frac{1}{M^{2L+1}}\right)\left(\frac{\Delta^2}{12}\right)} = \frac{3}{2} \frac{2L+1}{\pi^2 L} M^{2L+1}$$

Nyquist Converter:

The dynamic range of a N -bit Nyquist rate ADC is (now Δ becomes $\approx V_{REF}$ for large N),

$$DR^2 = \frac{\text{Maximum signal power}}{S_Q} = \frac{(V_{REF}/2\sqrt{2})^2}{\Delta^2/12} = \frac{3}{2} 2^{2N} \quad \rightarrow \quad DR = \sqrt{1.5} 2^N$$

Expressing DR in terms of dB (DR_{dB}) and solving for N , gives

$$N = \frac{DR_{dB} - 1.7609}{6.0206} \quad \text{or} \quad DR_{dB} = (6.0206N + 1.7609) \text{ dB}$$

Example: A 16-bit $\Delta\Sigma$ ADC requires about 98dB of dynamic range. For a second-order modulator, M must be 153 or 256 since we must use powers of 2.

Therefore, if the bandwidth is 20kHz, then the clock frequency must be 10.24MHz.

Multibit Quantizers

A single-bit quantizer:

$$\Delta = V_{REF}$$




Advantage is that the DAC is inherently linear.

Multi-bit quantizer:

Consists of an ADC and DAC of B-bits.

$$\Delta = \frac{V_{REF}}{2^{B-1}}$$

   Disadvantage is that the DAC is no longer perfectly linear. To get large resolution delta-sigma ADCs requires highly precise DACs.



Dynamic range of a multibit $\Delta\Sigma$ ADC:

$$DR^2 = \frac{3}{2} \frac{2^{L+1}}{\pi^{2L}} M^{2L+1} (2^{B-1})^2$$

Example 39-1 - Tradeoff Between Signal Bandwidth and Accuracy of $\Delta\Sigma$ ADCs

Find the minimum oversampling ratio, M , for a 16-bit oversampled ADC which uses (a.) a 1-bit quantizer and third-order loop, (b.) a 2-bit quantizer and third-order loop, and (c.) a 3-bit quantizer and second-order loop. For each case, find the bandwidth of the ADC if the clock frequency is 10MHz.

Solution

We see that 16-bit ADC corresponds to a dynamic range of approximately 98dB.

(a.) Solving for M gives

$$M = \left(\frac{2}{3} \frac{DR^2}{2L+1} \frac{\pi^{2L}}{(2B-1)^2} \right)^{1/(2L+1)}$$

Converting the dynamic range to 79,433 and substituting into the above equation gives a minimum oversampling ratio of $M = 48.03$ which would correspond to an oversampling rate of 64. Using the definition of M as $f_c/2f_B$ gives f_B as $10\text{MHz}/2 \cdot 64 = 78\text{kHz}$.

(b.) and (c.) For part (b.) and (c.) we obtain a minimum oversampling rates of $M = 32.53$ and 96.48, respectively. These values correspond to oversampling rates of 32 and 128, respectively. The bandwidth of the converters is 312kHz for (b.) and 78kHz for (c.).

Z-Domain Equivalent Circuits

The modulator structures are much easier to analyze and interpret in the z-domain.

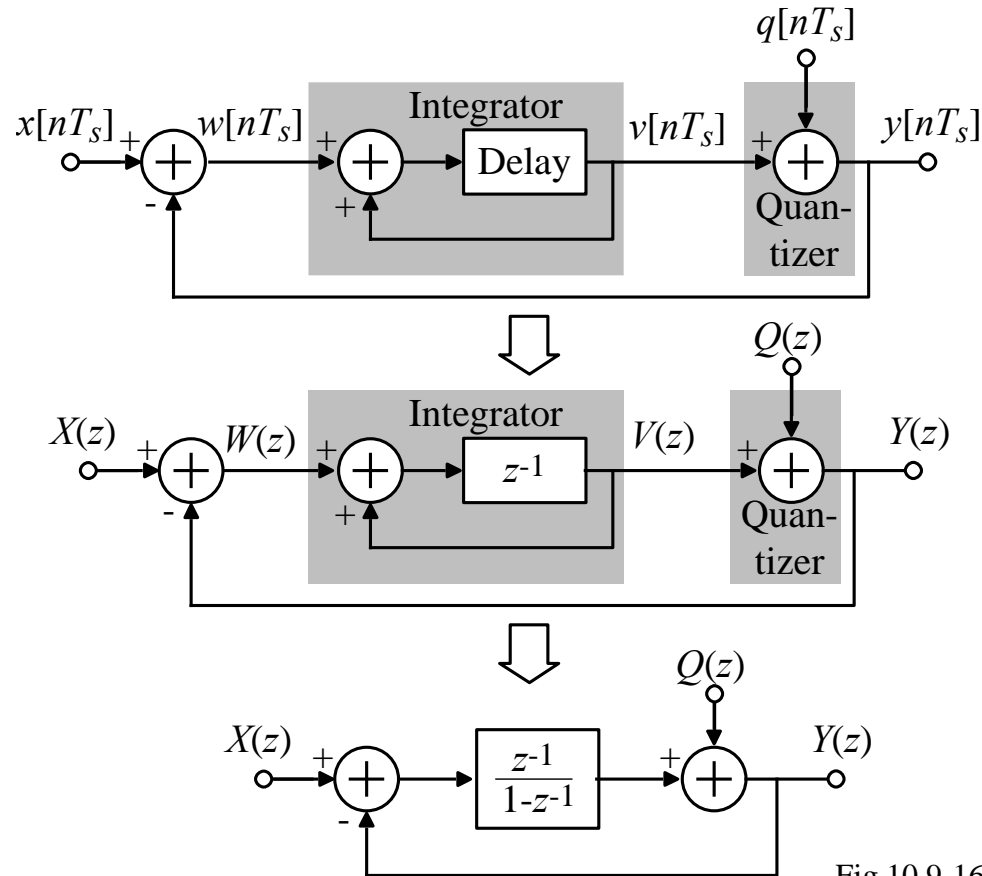


Fig.10.9-16

$$Y(z) = Q(z) + \left(\frac{z^{-1}}{1-z^{-1}} \right) [X(z) - Y(z)] \quad \rightarrow \quad Y(z) \left(\frac{1}{1-z^{-1}} \right) = Q(z) + \left(\frac{z^{-1}}{1-z^{-1}} \right) X(z)$$

$$\therefore Y(z) = (1-z^{-1})Q(z) + z^{-1}X(z) \quad \rightarrow \quad NTF_Q(z) = (1-z^{-1}) \quad \text{for } L = 1$$

Cascaded, Second-Order $\Delta\Sigma$ Modulator

Since the single-loop architecture with order higher than 2 are unstable, it is necessary to find alternative architectures that allow stable higher order modulators.

A cascaded, second-order structure:

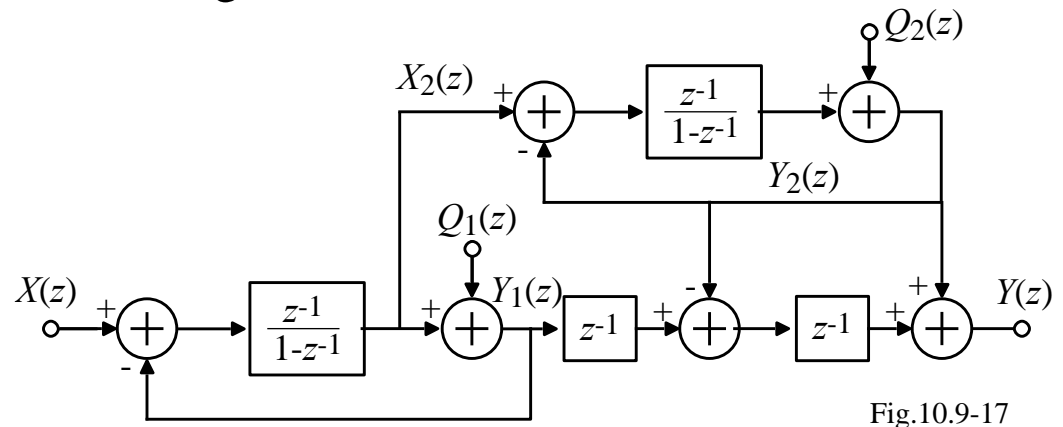


Fig.10.9-17

$$Y_1(z) = (1-z^{-1})Q_1(z) + z^{-1}X(z)$$

$$X_2(z) = \left(\frac{z^{-1}}{1-z^{-1}} \right) (X(z) - Y_1(z))$$

$$= \left(\frac{z^{-1}}{1-z^{-1}} \right) X(z) - \left(\frac{z^{-1}}{1-z^{-1}} \right) [(1-z^{-1})Q_1(z) + z^{-1}X(z)]$$

$$Y_2(z) = (1-z^{-1})Q_2(z) + z^{-1}X_2(z) = (1-z^{-1})Q_2(z) + \left(\frac{z^{-2}}{1-z^{-1}} \right) X(z) - z^{-2}Q_1(z) - \left(\frac{z^{-2}}{1-z^{-1}} \right) X(z)$$

$$= (1-z^{-1})Q_2(z) - z^{-2}Q_1(z)$$

$$Y(z) = Y_2(z) - z^{-1}Y_2(z) + z^{-2}Y_1(z) = (1-z^{-1})Y_2(z) + z^{-2}Y_1(z)$$

$$= (1-z^{-1})^2 Q_2(z) - (1-z^{-1})z^{-2}Q_1(z) + (1-z^{-1})z^{-2}Q_1(z) + z^{-3}X(z) = (1-z^{-1})^2 Q_2(z) + z^{-3}X(z)$$

$$\therefore Y(z) = (1-z^{-1})^2 Q_2(z) + z^{-3}X(z)$$

Third-Order, MASH $\Delta\Sigma$ Modulator

It can be shown that

$$Y(z) = X(z) + (1-z^{-1})^3 Q_3(z)$$

This results in a 3rd-order noise shaping and no delay between the input and output.


 


Fig. 10.9-17A

Comments:

- The above structures that eliminate the noise of all quantizers except the last are called *MASH* or multistage architectures.
- Digital error cancellation logic is used to remove the quantization noise of all stages, except that of the last one.

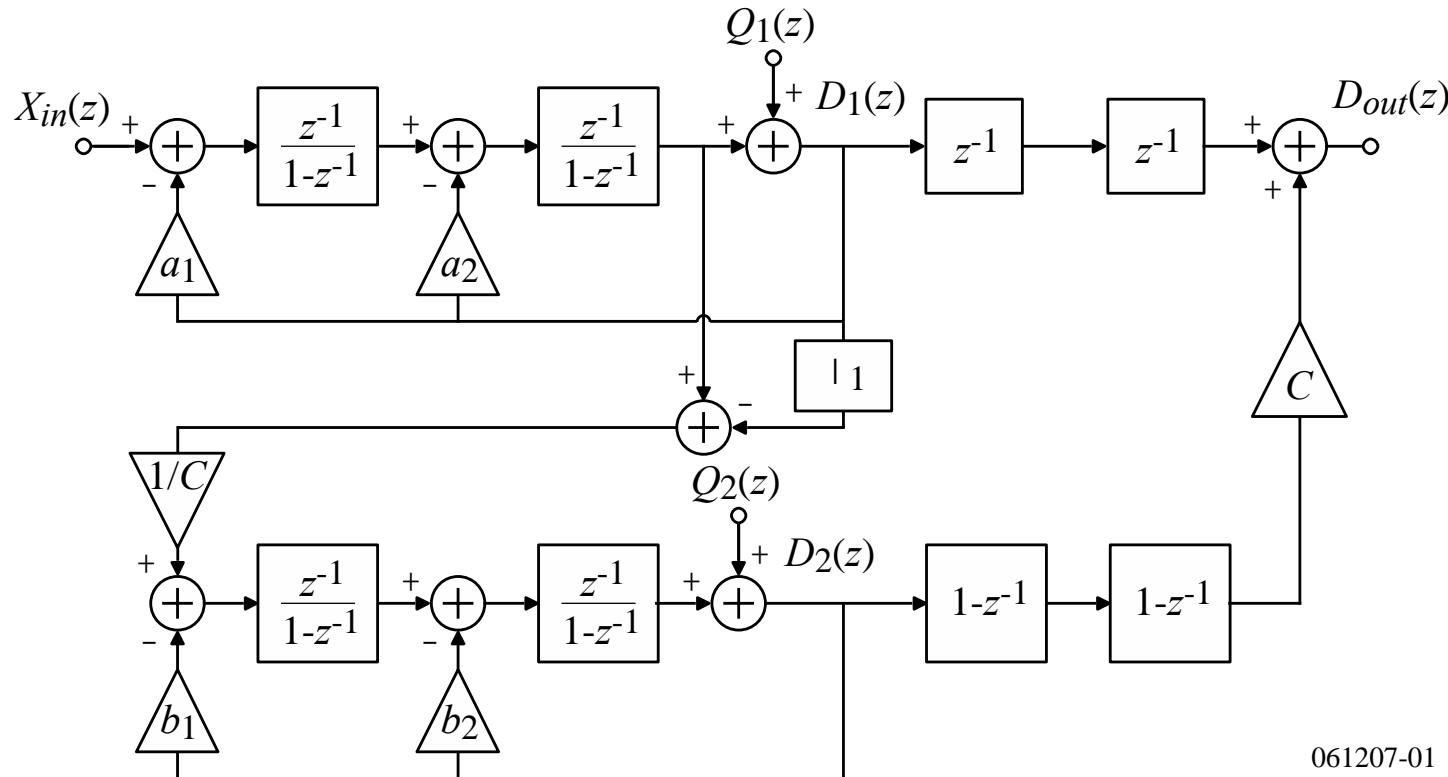A Fourth-Order, MASH-type Modulator using Scaling of Error Signals†



The signal is divided by $1/C$ as it passes from the first 2nd-order modulator to the second 2nd-order modulator. The digital output of the second 2nd-order modulator is then multiplied by the inverse factor of C .

061207-01


The various transfer functions are ($a_1=1$, $a_2=2$, $b_1=1$, $b_2=2$, $\lambda_1=2$ and $C=4$) :

$$D_1(z) = X_{in}(z) + (1-z^{-1})^2 Q_1(z) \quad \text{and} \quad D_2(z) = (1/C)(-Q_1(z)) + (1-z^{-1})^2 Q_2(z)$$


$$\text{Giving} \quad D_{out}(z) = X_{in}(z) + (1-z^{-1})^4 Q_2(z)$$

† U.S. Patent 5,061,928, Oct. 29, 1991.
CMOS Analog Circuit Design

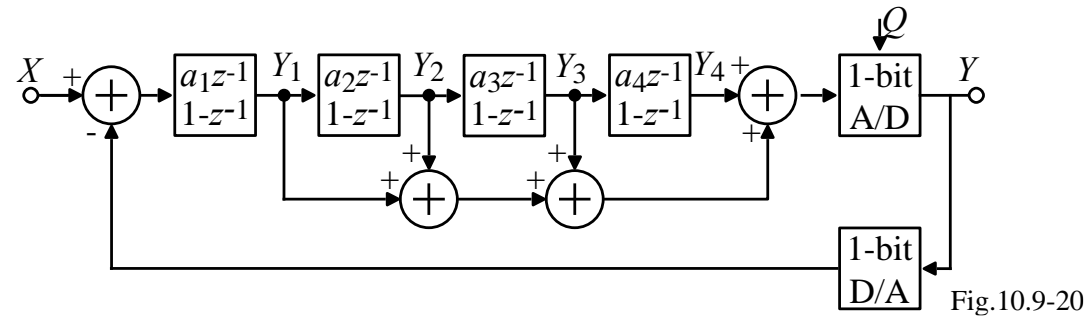
Distributed Feedback $\Delta\Sigma$ Modulator - Fourth-Order




Amplitude of integrator outputs:

 

 Distributed Feedback $\Delta\Sigma$ Modulator - Fourth-Order – Continued



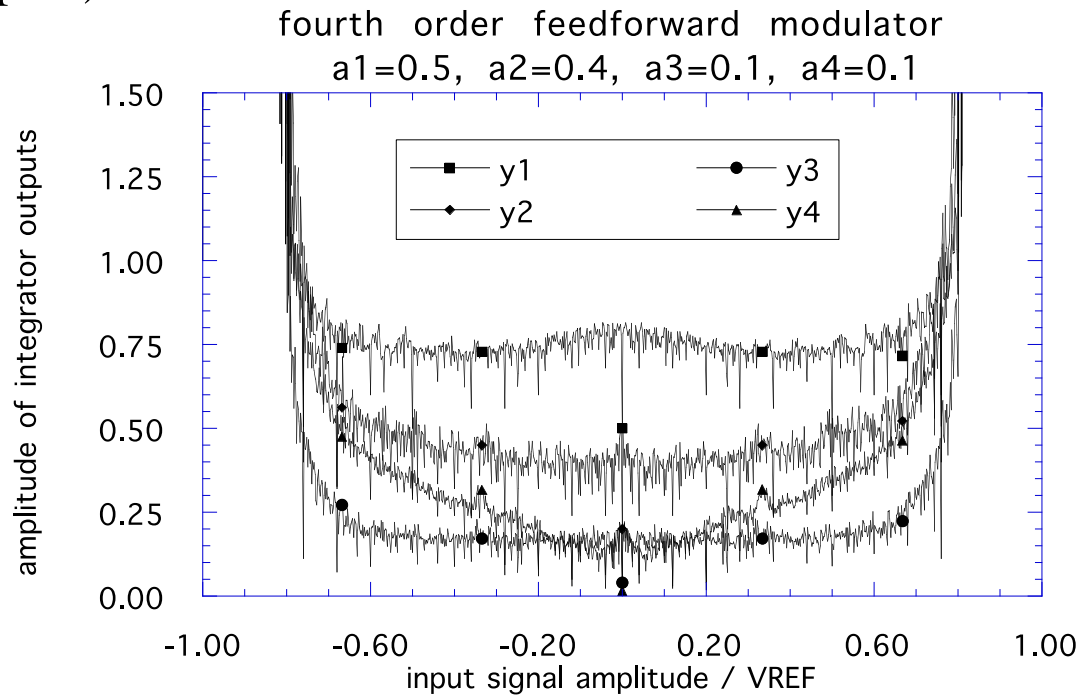Amplitude of integrator outputs (Integrator constants have been optimized to minimize the integrator outputs):



Cascaded of a Second-Order Modulator with a First-Order Modulator

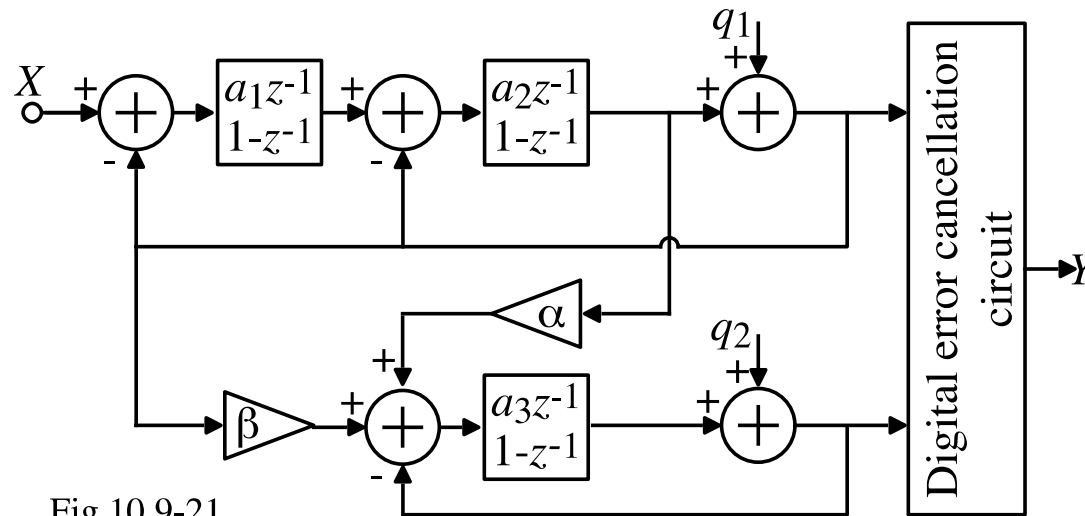


Fig.10.9-21

Comments:

- The stability is guaranteed for cascaded structures
- The maximum input range is almost equal to the reference voltage level for the cascaded structures
- All structures are sensitive to the circuit imperfection of the first stages
- The output of cascaded structures is multi-bit requiring a more complex digital decimator

Integrator Circuits for $\Delta\Sigma$ Modulators

Fundamental block of the $\Delta\Sigma$ modulator:

 


Fig.10.9-22

Fully-Differential, Switched Capacitor Implementation:

It can be shown that (Chapter 9 of the second edition or Appendix E of the third edition) that,

$$\frac{V_{out}(z)}{V_{in}(z)} = \left(\frac{C_s}{C_i}\right) \left(\frac{z^{-1}}{1-z^{-1}}\right)$$

becomes,

$$\frac{V_{out}^o(e^{j\omega T})}{V_{in}^o(e^{j\omega T})} = \left(\frac{C_1}{C_2}\right) \frac{e^{-j\omega T/2}}{j2 \sin(\omega T/2)} \left(\frac{\omega T}{\omega T}\right) = \left(\frac{C_1}{j\omega T C_2}\right) \left(\frac{\omega T/2}{\sin(\omega T/2)}\right) (e^{-j\omega T/2})$$

or

$$\frac{V_{out}^o(e^{j\omega T})}{V_{in}^o(e^{j\omega T})} = (\text{Ideal}) \times (\text{Magnitude error}) \times (\text{Phase error}) \text{ where } \omega_I = \frac{C_1}{TC_2} \Rightarrow \text{Ideal} = \frac{\omega_I}{j\omega}$$

 


Fig.10.9-23

Power Dissipation versus Supply Voltage and Oversampling Ratio

The following is based on the above switched-capacitor integrator:

1.) Dynamic range:

The noise in the band $[-f_s, f_s]$ is kT/C while the noise in the band $[-f_s/2M, f_s/2M]$ is kT/MC . We must multiply this noise by 4; x2 for the sampling and integrating phases and x2 for differential operation. The dynamic range is then V_{DD} divided by this noise,

$$\therefore DR = \frac{V_{DD}^2/2}{4kT/MC_s} = \frac{V_{DD}^2 MC_s}{8kT}$$

2.) Lower bound on the sampling capacitor, C_s , can be written as: $C_s = \frac{8kT \cdot DR}{V_{DD}^2 M}$

3.) Static power dissipation of the integrator: $P_{int} = I_b V_{DD}$

4.) Settling time for a step input of $V_{o,max}$:

$$I_b = C_i \frac{V_{o,max}}{T_{settle}} = \left(\frac{C_i}{T_{settle}} \right) \left(\frac{C_s}{C_i} V_{DD} \right) = \frac{C_s V_{DD}}{T_{settle}} = C_s V_{DD} (2f_s) = 2M f_N C_s V_{DD}$$

$$\therefore P_{int} = 2M f_N C_s V_{DD}^2 = 16kT \cdot DR \cdot f_N$$

Because of additional feedback to the 1st integrator, power is increased by a factor of 2.

$$\therefore P_{1st-int} = 32kT \cdot DR \cdot f_N$$

SUMMARY

- Oversampled ADCs allow signal bandwidth to be efficiently traded for resolution
- Noise shaping oversampled ADCs preserve the signal spectrum and shape the noise quantization spectrum
- The modulator shapes the noise quantization spectrum with a high pass filter
- The quantizer can be single or multiple bit
 - Single bit quantizers do not require linear DACs because a 1 bit DAC cannot be nonlinear
 - Multiple bit quantizers require ultra linear DACs
- Modulators consist of combined integrators with the goal of high-pass shaping of the noise spectrum and cancellation of all quantizer noise but the last quantizer