

LECTURE 3 – SIMULATION AND MEASUREMENT OF OP AMPS

Topics:

- Simulation versus measurement
- Different approaches to measure and simulate
 - Differential mode gain
 - Common mode rejection ratio
 - Power supply rejection ratio
 - Input offset voltage
 - Output voltage swing
 - Input common mode range
 - Slew rate and phase margin

What will I learn?

- How to do simulation and measurement of op amps

Dr. Phillip Allen

Prof. Emeritus, ECE, Georgia Tech

Version 181213

Simulation vs. Measurement

Comparison:

Objectives:

- The objective of simulation is to verify and optimize the design.
- The objective of measurement is to experimentally confirm the specifications.

Similarity between Simulation and Measurement:

- Same goals
- Same approach or technique

Differences between Simulation and Measurement:

- Simulation can idealize a circuit
 - All transistor electrical parameters are ideally matched
 - Ideal stimuli
- Measurement must consider all nonidealities
 - Physical and electrical parameter mismatches
 - Non-ideal stimuli
 - Parasitics

Differential Mode Gain

Low frequency gain, GB, and Phase Margin:

If the op amp has a large differential voltage gain, it cannot operate without negative feedback to establish the operating point.



Simulation:

- L and C should be selected large enough so that $1/\sqrt{LC}$ is greater than the lowest frequency of interest.
- Some simulators (not NGSpice) have the ability to measure the open loop by inserting a voltage in series with the feedback loop.

Measurement:

Drive the output at the desired operating point and measure the input response.
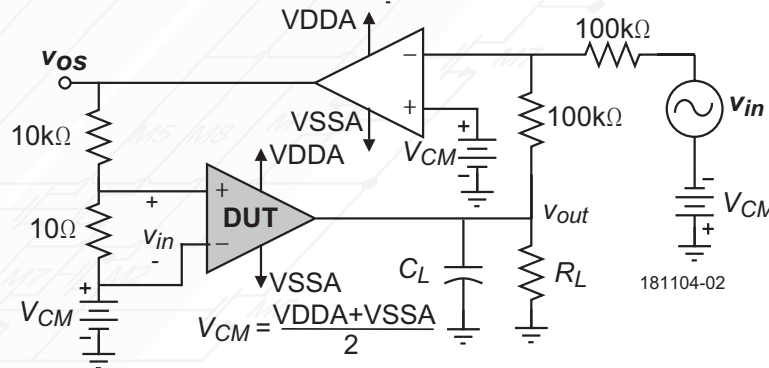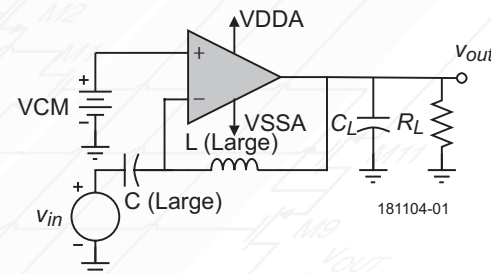
$$\frac{v_{out}}{v_{in}} = \frac{v_{in}}{v_{OS}/1000} = 1000 \times \frac{v_{in}}{v_{OS}}$$



Common Mode Rejection Ratio

CMRR:

- Definition


$$CMRR = \left| \frac{A_{vd}}{A_{cm}} \right| = \frac{\left(\frac{v_{out}}{v_{id}} \right)}{\left(\frac{v_{out}}{v_{icm}} \right)}$$

- Simulation


$$|CMRR| = \frac{V_{cm}}{V_{out}}$$

- Measurement
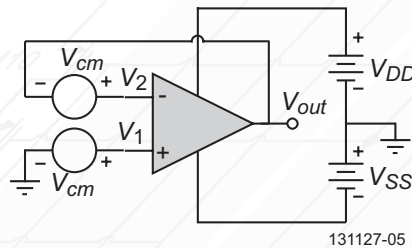
$$CMRR = \frac{v_{out}/v_{in}}{v_{out}/v_{icm}} = \frac{v_{icm}}{v_{in}} = 1000 \times \frac{v_{icm}}{v_{OS}}$$



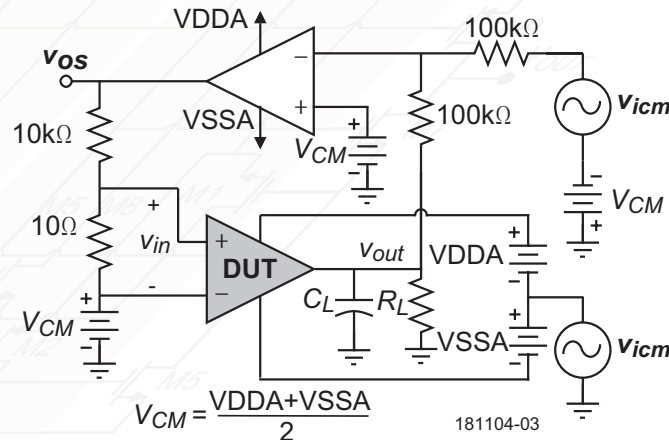Works only if the op amp is perfectly matched.




Power Supply Rejection Ratio

PSRR:

- Definition

$$PSRR^+ = \left| \frac{A_{vd}}{A_{dd}} \right| = \frac{(v_{out}/v_{id})}{(v_{out}/v_{dd})} \quad \text{and} \quad PSRR^- = \left| \frac{A_{vd}}{A_{ss}} \right| = \frac{(v_{out}/v_{id})}{(v_{out}/v_{ss})}$$

- Simulation

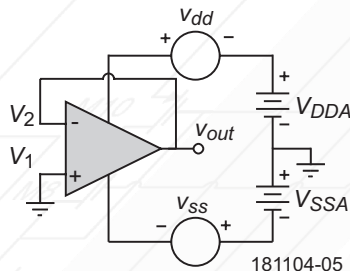


- Measurement

$$PSRR^+ = \frac{v_{out}/v_{in}}{v_{out}/v_{dd}} = \frac{v_{dd}}{v_{in}} = 1000 \times \frac{v_{dd}}{v_{os}}$$

$$PSRR^- = \frac{v_{out}/v_{in}}{v_{out}/v_{ss}} = \frac{v_{ss}}{v_{in}} = 1000 \times \frac{v_{ss}}{v_{os}}$$
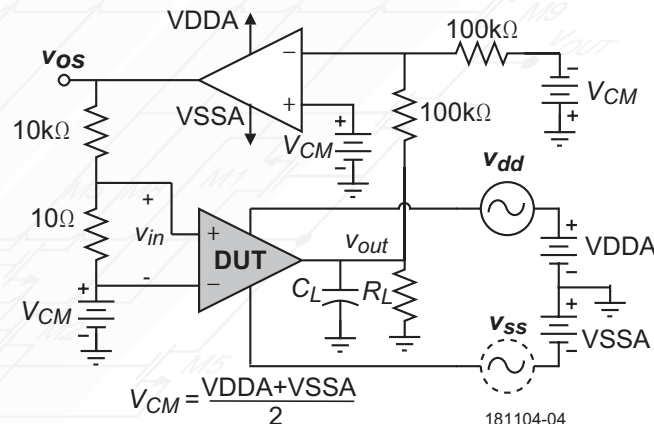
$$PSRR^+ = \frac{A_v}{A_{dd}} = \frac{v_{dd}}{v_{out}} \quad \text{or} \quad PSRR^- = \frac{A_v}{A_{ss}} = \frac{v_{ss}}{v_{out}}$$



Input Offset Voltage

V_{OS} :



- Definition

$$V_{OS} = \frac{V_{out}(V_{in}=0)}{A_{vd}}$$

- Simulation/Measurement



- Closed loop

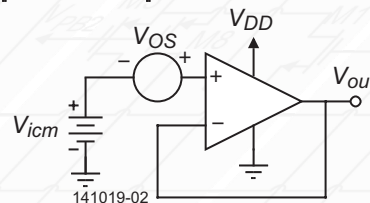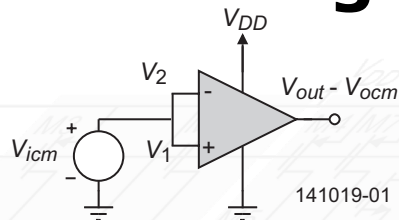Watch out for gain error masking the input offset voltage



$$V_{out} = \left(\frac{A_{vd}}{1 + A_{vd}} \right) (V_{icm} + V_{OS}) \rightarrow V_{out} = V_{icm} + \left[\left(\frac{A_{vd}}{1 + A_{vd}} \right) V_{OS} - \frac{V_{icm}}{1 + A_{vd}} \right] = V_{icm} + "V_{OS}"$$


- Open loop

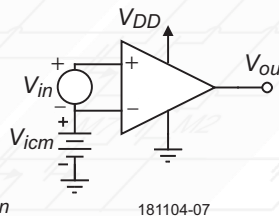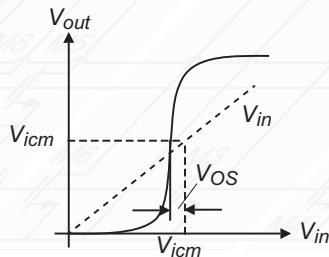

Output Voltage Swing

$V_{out(max)}$ and $V_{out(min)}$:

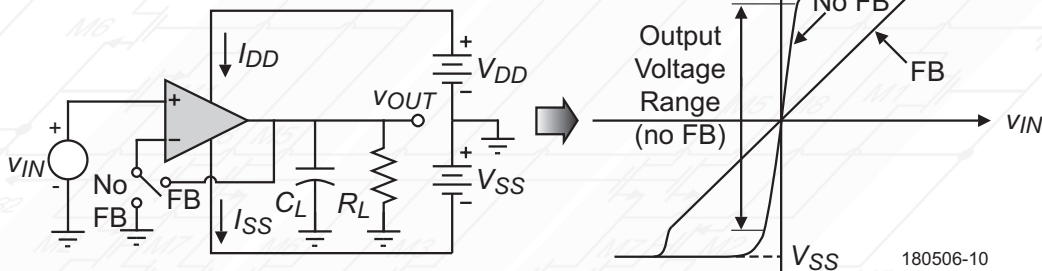- Definition
 - The output voltage swing is the range of output voltages over which the slope of the transfer curve remains constant.
 - However, with feedback this range is extended because feedback linearizes the transfer function
- Measurement/Simulation




Input Common Mode Voltage Range

ICMR:

Definitions

1. ICMR is the range of input common-mode voltage over which the differential amplifier will continue to sense and amplify the difference signal with the same gain.
2. ICMR is the input common-mode voltage range over which all pertinent MOSFETs remain in the saturation region.

Simulation/Measurement

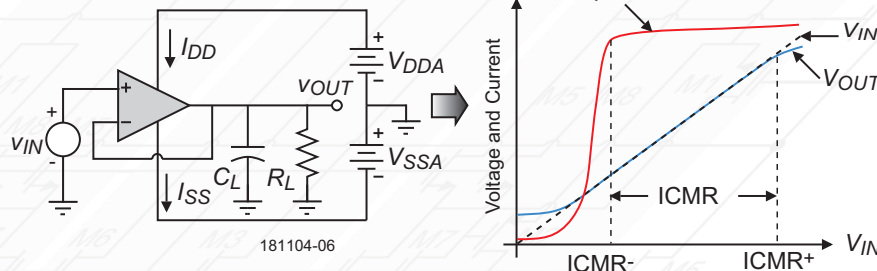

Also, plot the current in the input stage or the power supply current.



Input Common Mode Voltage Range – Cont'd

ICMR – An alternative approach:

Simulation:

Vary the input common mode voltage (V_{CM}) and measure the open loop gain. When the gain goes below some predefined value (i.e. 20dB), this would define the upper and lower ICMR.

Measurement:

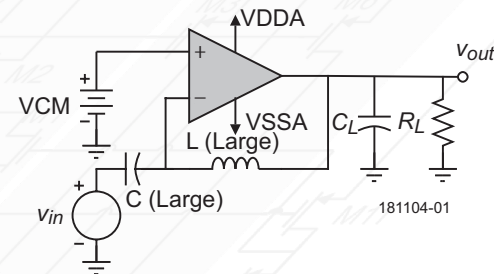
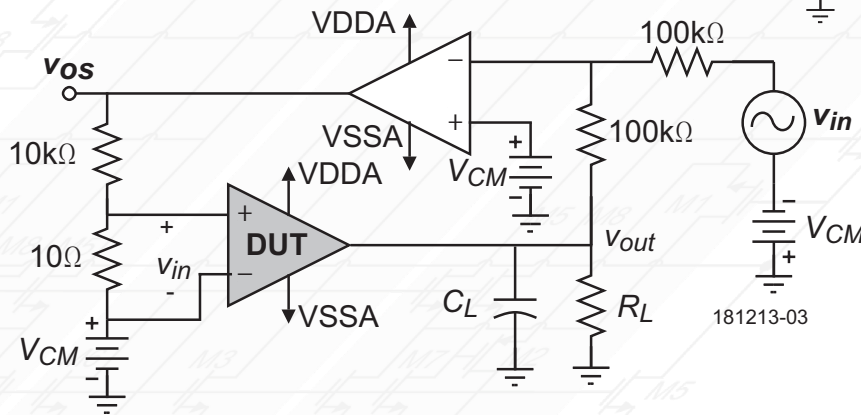


Slew Rate

SR:

Simulation/Measurement:

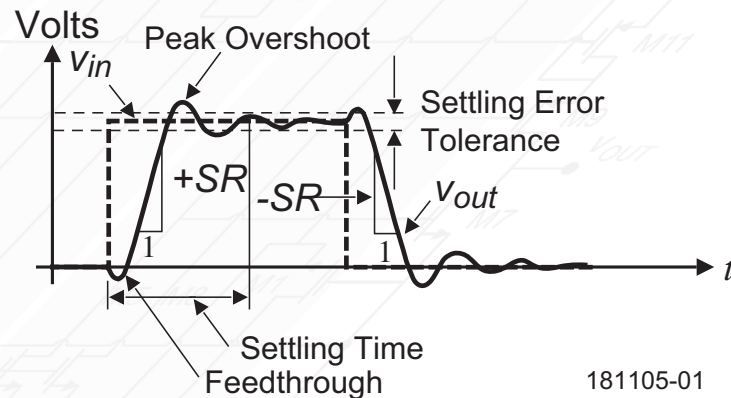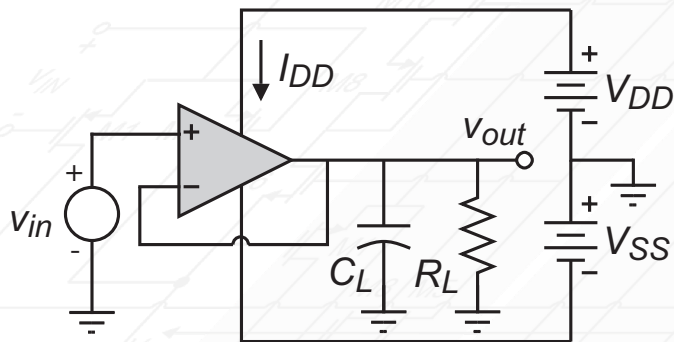Put the op amp in the unity gain configuration and apply a positive and negative step within the ICMR range.





181105-01

Phase Margin

PM:

Simulation/Measurement

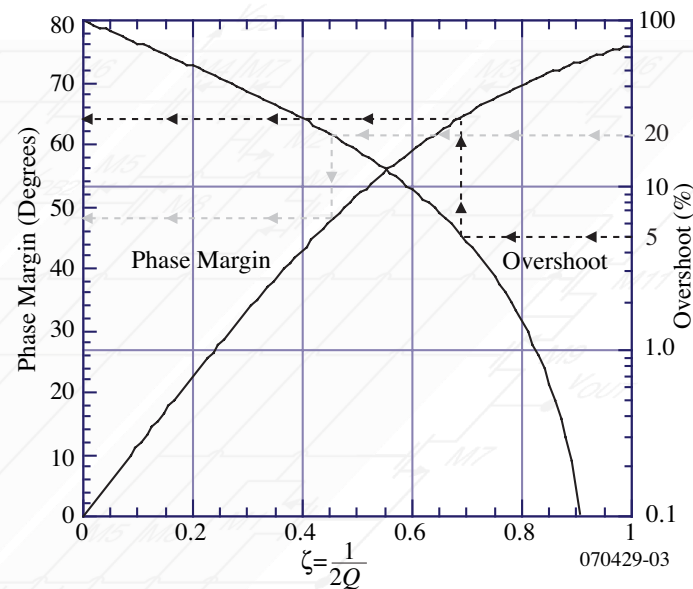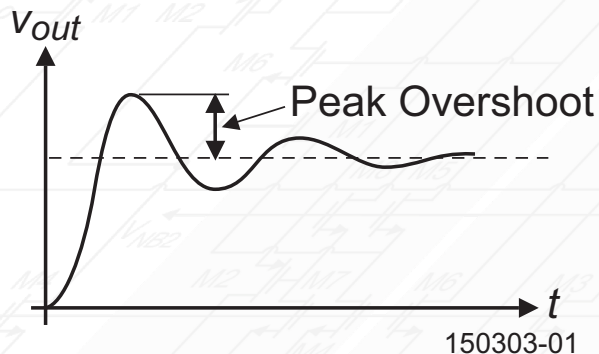If the unity gain configuration can be approximated as a low frequency pole and a pole at $-GB$, then for a non-slewing step response, the peak overshoot can be related to the phase margin.



$$PM(Deg) = 57.2958 \cos^{-1} \left[\sqrt{4\zeta^4 + 1} - 2\zeta^2 \right]$$

$$Overshoot (\%) = 100 \exp \left(\frac{-\pi\zeta}{\sqrt{1 - \zeta^2}} \right)$$

Simulation and Measurement of Op Amps

Summary:

- Simulation versus measurement
- Differential mode gain
- Common mode rejection ratio
- Power supply rejection ratio
- Input offset voltage
- Output voltage swing
- Input common mode range
- Slew rate
- Phase margin

