

LECTURE 6 - HOW TO DESIGN DIFFERENTIAL OUTPUT OP AMPS

Topics:

- Introduction to differential output op amps
- Single stage differential output op amp design
- Folded cascode differential output op amp design
 - Class A
 - Class B
- Common mode stabilization
- Common mode feedback bandwidth

What will I learn?

- How to design op amps with a differential output to satisfy a given set of specifications

Dr. Phillip Allen

Prof. Emeritus, ECE, Georgia Tech

Version 190521

Differential Output Op Amp

Circuit Considerations

Symbol:

Definitions:

Differential input voltage = $v_{id} = v_{i1} - v_{i2}$


Differential output voltage = $v_{od} = v_{o1} - v_{o2}$

Differential in-out voltage gain = $A_{vdiff} = v_{od}/v_{id}$


Common mode input voltage = $v_{icm} = 0.5(v_{i1} + v_{i2})$

Common mode output voltage = $v_{ocm} = 0.5(v_{o1} + v_{o2})$

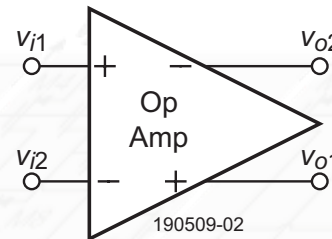
Common mode voltage gain = $A_{vcm} = v_{ocm}/v_{icm}$



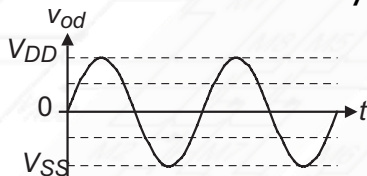
The challenge for differential output op amps is to control the dc value of V_{ocm} . Ideally, it should be midway between V_{DD} and V_{SS} .



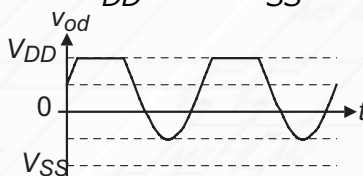CM output voltage properly defined,
 $V_{ocm} = 0$



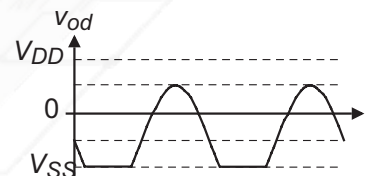CM output voltage too large,
 $V_{ocm} = 0.5V_{DD}$



CM output voltage too small,
 $V_{ocm} = 0.5V_{SS}$

070506-01

Single-Ended and Differential Loads

Differential Voltage Gain

Class A Loads:

- Differential Load

$$v_{od} = \frac{g_m R_L}{2} v_{id} \Rightarrow A_{vdiff} = \frac{g_m R_L}{2}$$

- Single-ended Loads

$$v_{od} = v_{o1} - v_{o2} = \left(\frac{g_m R_L}{4} + \frac{g_m R_L}{4} \right) v_{id}$$

$$\Rightarrow A_{vdiff} = \frac{g_m R_L}{2}$$

Class B Loads (Push-pull):


- Differential Load

$$v_{od} = g_m R_L v_{id} \Rightarrow A_{vdiff} = g_m R_L$$


- Single-ended Loads

$$v_{od} = v_{o1} - v_{o2} = \left(\frac{g_m R_L}{2} + \frac{g_m R_L}{2} \right) v_{id}$$


$$\Rightarrow A_{vdiff} = g_m R_L$$

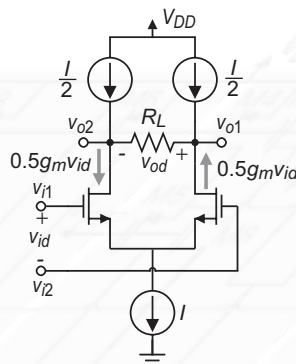


Differential Load

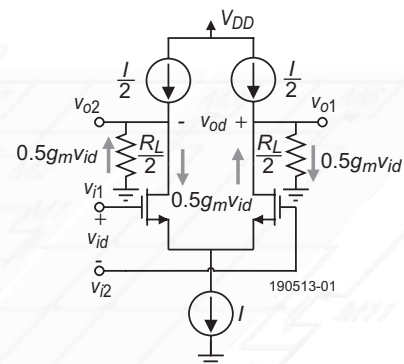

Single-Ended Loads

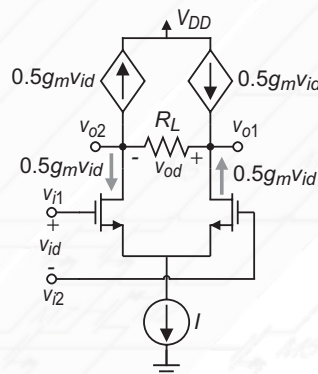

Differential Load

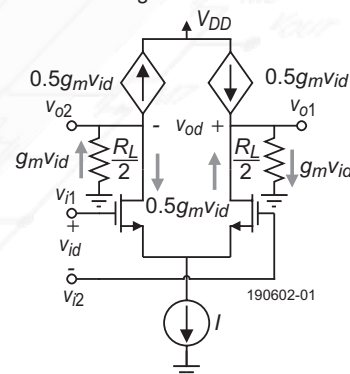

Single-Ended Loads

Single-Ended and Differential Loads

Slew Rate

Class A Loads:

- Differential Load

$$SR = \frac{I}{2C_L}$$

- Single-ended Loads

$$SR = SR_1 - SR_2 = \frac{I}{2} \times \frac{1}{2C_L} + \frac{I}{2} \times \frac{1}{2C_L} = \frac{I}{2C_L}$$


Class B Loads (Push-pull):

- Differential Load


$$SR = \frac{I}{C_L}$$

- Single-ended Loads

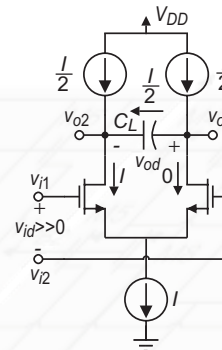
$$SR = SR_1 - SR_2 = I \times \frac{1}{2C_L} + I \times \frac{1}{2C_L} = \frac{I}{C_L}$$




Differential Load

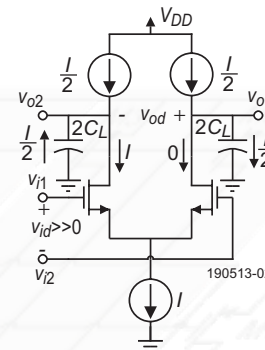

Single-Ended Loads

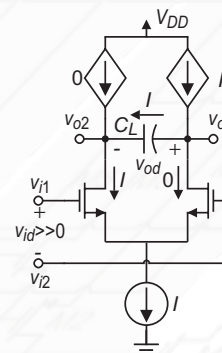

Differential Load

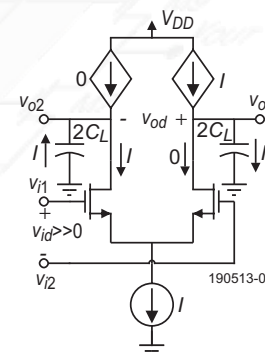

Single-Ended Loads

Output Common Mode Stabilization


Objective

The objective of the output common mode stabilization circuit is to maintain the desired output common mode voltage.

Output Common Mode Stabilization

Requirements:

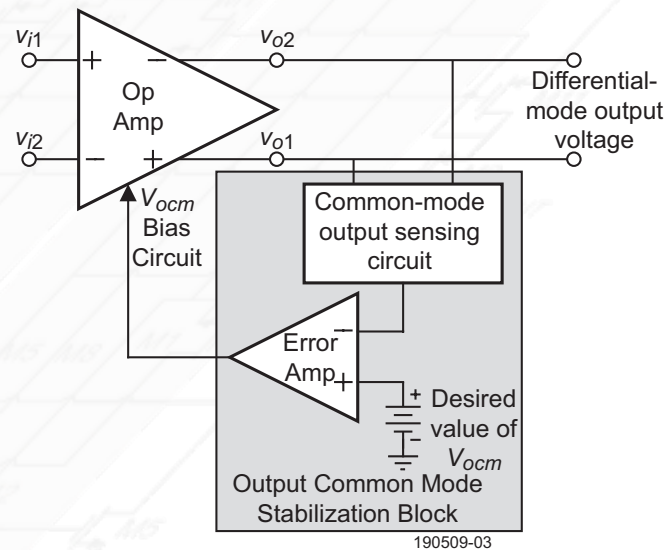- The common mode stabilization is a feedback circuit and must be negative and stable
- The output differential signal should have no influence on the common mode stabilization
- The common mode stabilization should not influence the output differential voltage (such as loading it)




Output Common Mode Sensing Circuits

Approaches



Resistive:

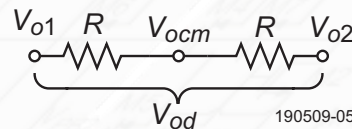- If R is not large, it may load the op amp




Transistor:

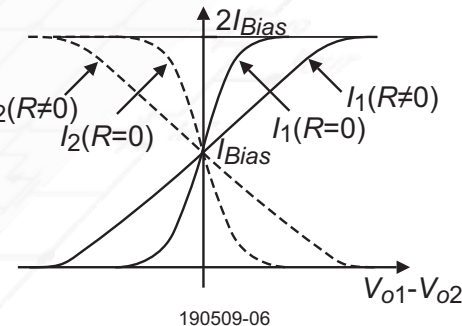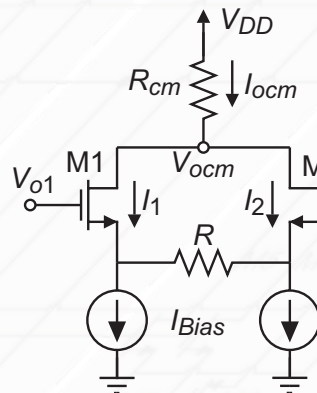- Does not load the op amp
- Can be NMOS or PMOS version
- The sum of I_1 and I_2 become a common mode current
- R allows a larger value of differential output voltage
- Can use V_{ocm} or I_{ocm} as the common mode output signal
- Could split R in two and use a single I_{Bias} current sink



Resistor CM Stabilization Circuit


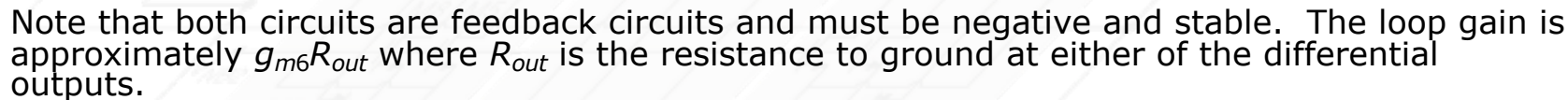


Also, the GB of the CM circuit (GB_{cm}) must be compatible with the GB of the amplifier (GB_{dm}). I.e., $GB_{dm} > GB_{cm}$, $GB_{dm} = GB_{cm}$, or $GB_{dm} < GB_{cm}$.

Single Stage, Class A, Differential Output Op Amp Design

Design Procedure – OA16

Step	Design Equations	Comments
1	Use Design Procedure OA1 to design M1-M5	M3 no longer has the gate connected to drain
2	$I_5 = 2 \times (SR \times C_L)$	Max. current through C_L is $0.5I_5$
3	Let $W_{10}/L_{10} = (I_{10}/I_5) \times W_5/L_5$	Choose I_{10} based on P_{diss}
4	Let $W_8/L_8 = W_9/L_9 = (I_6/I_1) \times W_3/L_3$	Choose I_6 and I_7 based on P_{diss}
5	$g_{m6} = g_{m7} = GB_{cm} \times C_L$, $\frac{W_6}{L_6} = \frac{g_m^2}{K'_6 I_{10}}$, $W_{7A}/L_{7A} = W_{7B}/L_{7B} = 0.5W_6/L_6$	Choose GB_{cm}
6	$R_2 = V_{ocm}/I_{R1}$	Select I_{R1} based on P_{diss}
7	$R_1 = (V_{DD}/I_{R1}) - R_2$	
8	If the output differential signal swing is too large, use the resistive common mode sampling circuit	

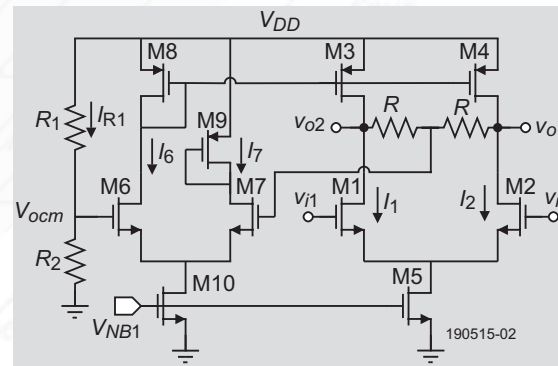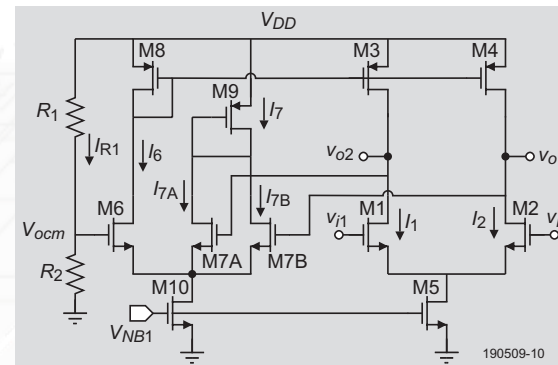


Single Stage, Class A, Differential Output Op Amp Design

Example 1:

If $K_N' = 120\mu\text{A}/\text{V}^2$, $K_P' = 25\mu\text{A}/\text{V}^2$, $V_{TN} = |V_{TP}| = 0.5\text{V}$, $\lambda_N = 0.06\text{V}^{-1}$, and $\lambda_P = 0.08\text{V}^{-1}$, use Design Procedure OA16 to design a one stage, Class A, differential output op amp. Assume that $C_L = 5\text{pF}$.

$A_{vdiff} > 50 \text{ V/V}$	$V_{DD} = 2.5\text{V}$	$GB = 10\text{MHz}$	$SR > 5\text{V}/\mu\text{s}$
Phase margin $\geq 60^\circ$	$1\text{V} \leq ICMR \leq 2\text{V}$	$P_{diss} \leq 1\text{mW}$	$V_{ocm} = 1.25\text{V}$

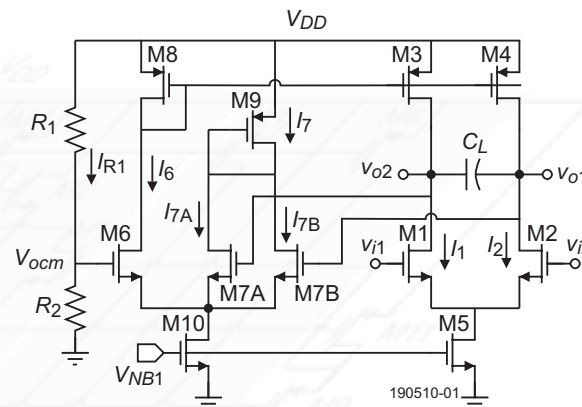

- 1.) $I_5 = 2 \times SR \times C_L = 2 \times 5\text{V}/\mu\text{s} \times 5\text{pF} = 50\mu\text{A}$, $P_{diss} = 2.5\text{V} \times 50\mu\text{A} = 0.125\text{mW}$
- 2.) $g_m = g_{m1} = g_{m2} = GB_{dm} \times C_L = 100\pi\mu\text{S}$, $\frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{g_m^2}{K_1' I_5} = \frac{314\mu\text{S}^2}{120 \times 10^{-6} \times 50\mu\text{A}} = 16.43 \rightarrow 16$
- 3.) $\frac{W_3}{L_3} = \frac{W_4}{L_4} = \frac{I_5}{K_1' [V_{DD} - ICMR^+ - |V_{T3}| + V_{T1}]^2} = \frac{50\mu\text{A}}{25 \times 10^{-6} [2.5 - 2 - 0.5 + 0.5]^2} = 4$
- 4.) $V_{GS1} = \sqrt{\frac{50\mu\text{A}}{120 \times 10^{-6} \times 16.43}} + 0.5 = 0.659$, $\frac{W_5}{L_5} = \frac{100\mu\text{A}}{120 \times 10^{-6} (1 - 0.659)^2} = 7.166 \rightarrow 7$
- 5.) $A_o = \frac{g_m R_L}{2} = \frac{2g_m}{(\lambda_N + \lambda_P) I_5} = \frac{2 \times 314\mu\text{S}}{(0.06 + 0.08) 50\mu\text{A}} = 97.42 (39.8\text{dB})$

Single Stage, Class A, Differential Output Op Amp Design

Example 1 - Continued:

6.) Choose $I_{10} = 50\mu\text{A} \Rightarrow P_{diss} = 0.250\text{mW}$


Therefore, $W_{10}/L_{10} = W_5/L_5$, and
 $W_8/L_8 = W_9/L_9 = W_3/L_3$.

7.) Let $GB_{cm} = GB_{dm}$. Therefore $W_6/L_6 = W_1/L_1$,
 $W_{7A}/L_{7A} = W_{7B}/L_{7B} = 0.5W_1/L_1$.

8.) Choose $I_{R1} = 10\mu\text{A} \Rightarrow P_{diss} = 0.275\text{mW}$

Therefore $R_1 = 2.5/10\mu\text{A} = 250\text{k}\Omega$ and $R_2 = 2.5/10\mu\text{A} = 250\text{k}\Omega$

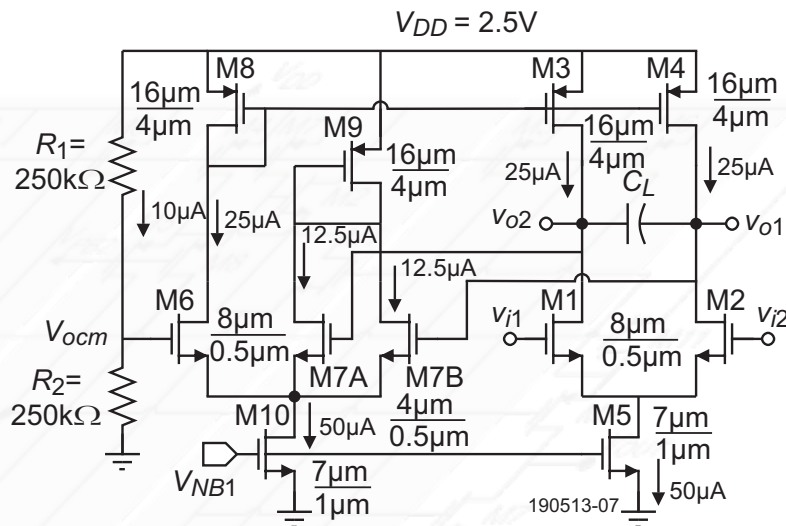9.) Design L 's and W 's/ Pick $L_1 = L_2 = L_6 = L_{7A} = L_{7B} = 0.5\mu\text{m}$ for speed. Therefore $W_1 = W_2 = W_6 = 8\mu\text{m}$, and $W_{7A} = W_{7B} = 8\mu\text{m}$. Pick $L_5 = L_{10} = 1\mu\text{m}$ which gives $W_5 = W_{10} = 7\mu\text{m}$. For PSRR and gain, let $L_3 = L_4 = L_8 = L_9 = 4\mu\text{m}$ which gives $W_3 = W_4 = W_8 = W_9 = 16\mu\text{m}$.



Design Procedure – 0A17

All gray arrows are $0.5g_m V_{id}$

Common mode Stabilization Circuit

Folded Cascode, Class A, Differential Output Op Amp Design

Example 2

Design a common mode stabilization circuit for the op amp designed in Example 3 of Lecture 1 (Single-Stage Op Amp Design) of Module 4 assuming $C_L = 5\text{pF}$.



- 1.) The design from Example 3 of Lecture 1 is shown.
- 2.) Choose $I_{16} = 100\mu\text{A}$ and $I_{R1} = 10\mu\text{A}$, therefore $P_{diss} = 2.5\text{V} \times (250\mu\text{A} + 100\mu\text{A} + 10\mu\text{A}) = 0.9\text{mW}$
- 3.) $W_{16}/L_{16} = (100\mu\text{A}/125\mu\text{A}) \times 160 = 128 \rightarrow 64\mu\text{m}/0.5\mu\text{m}$
- 4.) Choose $GB_{cm} = 1\text{MHz} \Rightarrow 20\pi \times 10^6$

$$\text{Therefore } \frac{W_{12}}{L_{12}} = \frac{g_m^2}{K'_1 I_{16}} = \frac{(62.8)^2}{25 \times 100} = 1.58 \rightarrow 2, \frac{W_{13A}}{L_{13A}} = \frac{W_{13B}}{L_{13B}} = 1$$

$$5.) \text{ Let } W_{14}/L_{14} = W_{15}/L_{15} = (75\mu\text{A}/50\mu\text{A}) W_{10}/L_{10} = 30$$

$$6.) R_1 = V_{OCM}/I_{R1} = 125\text{k}\Omega, R_2 = 250\text{k}\Omega - 125\text{k}\Omega = 125\text{k}\Omega$$

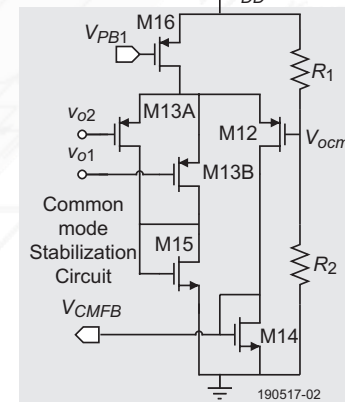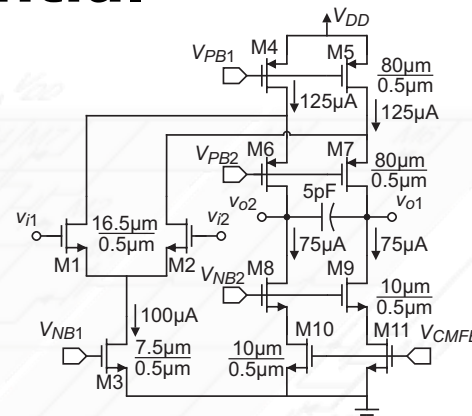
7.) Design W 's and L 's. Choose L_{12} and L_{13} as $1\mu\text{m}$ giving $W_{12} = 1\mu\text{m}$ and $W_{13A} = W_{13B} = 0.5\mu\text{m}$. Choose L_{14} and L_{15} as $1\mu\text{m}$ which gives $W_{14} = W_{15} = 15\mu\text{m}$.



Folded Cascode, Class B, Diff. Output Op Amp

Comments

- The folded-cascode op amp is desirable for class B implementation
- Two possible input circuits are shown
 - The one on the left has the advantage of a potentially large ICMR but the p -channel and n -channel inputs must be designed so the effective g_m is constant over the ICMR*
 - The one on the right is preferable if large ICMR is not needed.
- The previous CM stabilization circuits for Class A, folded-cascode op amp are applicable for the Class B, folded-cascode op amp


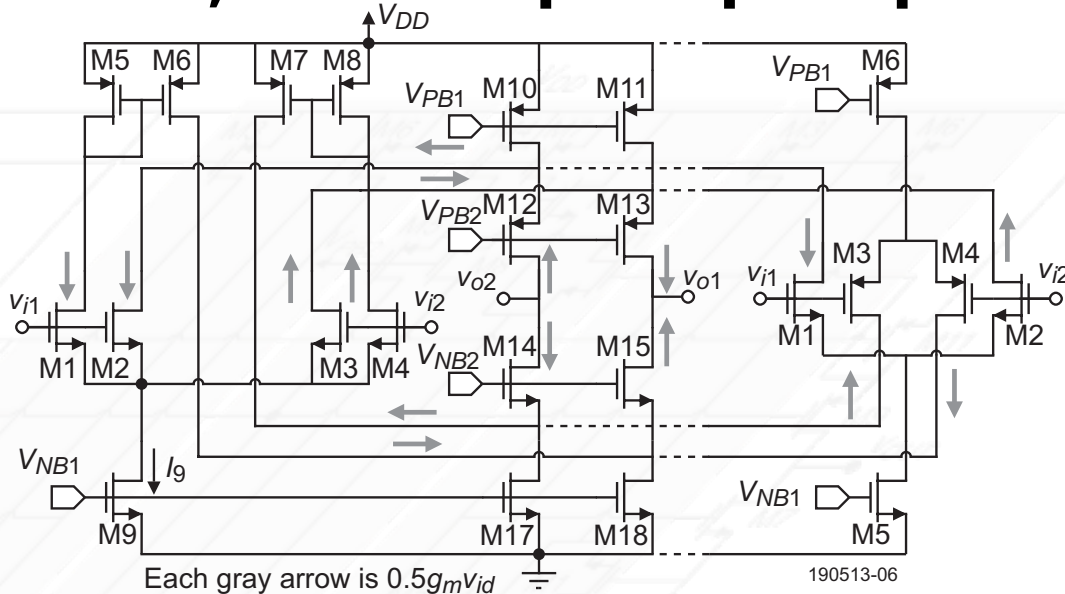


* R. Hogervorst et al., "CMOS Low-Voltage Operational Amplifiers with Constant- g_m Rail-to-Rail Input Stage," *Analog Integrated Circuits and Signal Processing*, Vol. 5, No. 4, pp. 135-146, March 1994.

Folded Cascode, Class B, Diff. Output Op Amp Design

Design Procedure – OA18

Step	Design Equations	Comments
1	$I_9 \geq 2 \cdot SR \cdot C_L$	Defines minimum current
2	$I_{10} = I_{11} = I_{16} = I_{17} = 0.5(1.1I_9 \text{ to } 1.5I_9) = 0.55I_9 \text{ to } 0.75I_9$	Avoids cascode current = 0
3	$W_{10}/L_{10} = W_{11}/L_{11} = 2I_{11}/[K'_P V_{SD4}(\text{sat})^2]$	$V_{SD11}(\text{sat}) = 0.5[V_{DD} - V_{out}(\text{max})]$
4	$W_{12}/L_{12} = W_{13}/L_{13} = 2I_{11}/[K'_P V_{SD6}(\text{sat})^2]$	$V_{SD13}(\text{sat}) = 0.5[V_{DD} - V_{out}(\text{max})]$
5	$\frac{W_{14}}{L_{14}} = \frac{W_{15}}{L_{15}} = \frac{W_{16}}{L_{16}} = \frac{W_{17}}{L_{17}} = \frac{2I_{17}}{K'_N V_{DS17}(\text{sat})^2}$	$V_{DS16}(\text{sat}) = 0.5[V_{out}(\text{min}) - V_{SS}]$
6	$g_{m1} = GB_{dm} \times C_L \rightarrow W_1/L_1 = W_2/L_2 = W_3/L_3 = W_4/L_4 = \frac{4GB_{dm}^2 C_L^2}{K'_N I_9}$	GB_{dm} is in rads/sec
7	$\frac{W_9}{L_9} = \frac{2I_9}{K'_N (ICMR^- - V_{GS1})^2}, V_{GS1} = \sqrt{i_9 / 2K'_N (\frac{W_1}{L_1})} + V_{T1}$	Note that $ICMR^-$ must be greater than V_{GS1}
8	$\frac{W_5}{L_5} = \frac{W_6}{L_6} = \frac{W_7}{L_7} = \frac{W_8}{L_8} = \frac{I_5}{K'_5 [V_{DD} - ICMR^+ - V_{T5} + V_{T1}]^2}$	$ICMR^+ = V_{in}(\text{max})$ specified, $M5 = M6 = M7 = M8$
9	Design the common stabilization circuit using steps 2-6 of Design Procedure OA17	
10	Check gain and power dissipation and iterate if necessary $A_o = g_{m1} R_{out}$ and $P_{diss} = (V_{DD} - V_{SS})(I_4 + I_5 + I_{22} + I_{R1})$	

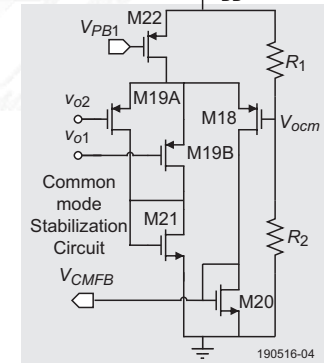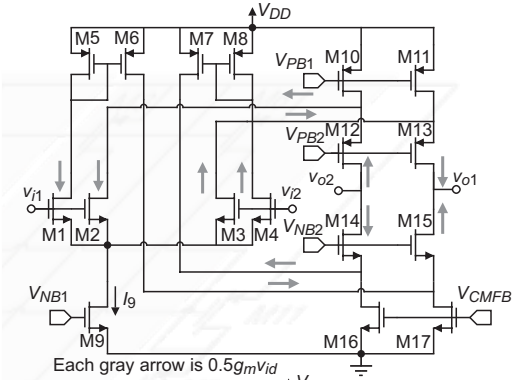



Folded Cascode, Class B, Diff. Output Op Amp Design

Example 3:

If $K_N' = 120\mu\text{A}/\text{V}^2$, $K_P' = 25\mu\text{A}/\text{V}^2$, $V_{TN} = |V_{TP}| = 0.5\text{V}$, $\lambda_N = 0.06\text{V}^{-1}$, and $\lambda_P = 0.08\text{V}^{-1}$, use Design Procedure OA18 to design a folded-cascode, Class B, differential output op amp. Assume that $C_L = 10\text{pF}$.

$A_{vdiff} > 5000 \text{ V/V}$	$V_{DD} = 2.5\text{V}$	$GB = 10\text{MHz}$	$SR > 5\text{V}/\mu\text{s}$	$P_{diss} \leq 1\text{mW}$
$PM \geq 60^\circ$	$1\text{V} \leq ICMR \leq 2\text{V}$	$V_{ocm} = 1.25\text{V}$	$V_o(\text{max}) = 2\text{V}$	$V_o(\text{min}) = 0.5\text{V}$

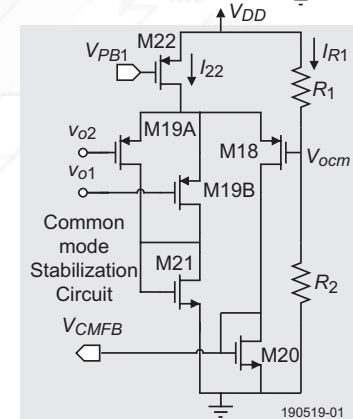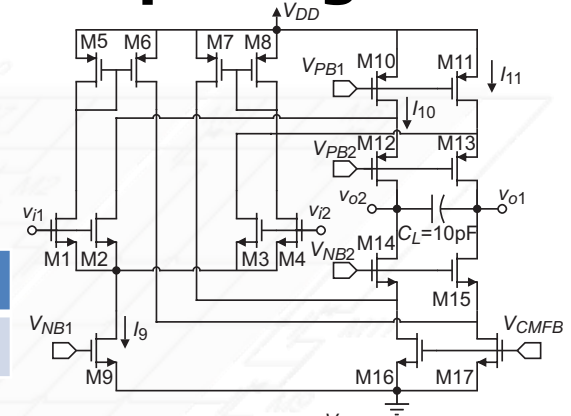- 1.) $I_9 = 2 \times SR \times C_L = 2 \times 5\text{V}/\mu\text{s} \times 10\text{pF} = 100\mu\text{A}$,
- 2.) Select $I_{10} = I_{11} = I_{16} = I_{17} = 125\mu\text{A}$, $P_{diss} = 2.5\text{V} \times 250\mu\text{A} = 0.250\text{mW}$
- 3.) V_{DSat} of M10 and M11 = 0.25V for gives $\frac{W_{10}}{L_{10}} = \frac{W_{11}}{L_{11}} = \frac{2 \times 125}{25 \times 0.25^2} = \underline{160}$
- 4.) Assuming $I_{12} = 125\mu\text{A}$ gives 160 for W_{12}/L_{12} and W_{13}/L_{13} .
- 5.) $V_{DS16}(\text{sat}) = 0.25\text{V} \rightarrow \frac{W_{14}}{L_{14}} = \frac{W_{15}}{L_{15}} = \frac{W_{16}}{L_{16}} = \frac{W_{17}}{L_{17}} = \frac{2I_{16}}{K_N' V_{DS16}(\text{sat})^2} = \frac{2 \times 125}{120 \times 0.25^2} = \underline{20}$
- 6.) $\frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{W_3}{L_3} = \frac{W_4}{L_4} = \frac{4GB^2 C_L^2}{K_N' I_9} = \frac{4(20\pi)^2 \times 10^2}{120 \times 100} \approx \underline{132}$
- 7.) $V_{DS9}(\text{sat}) = 0.5 - \sqrt{\frac{50}{120 \times 132}} = 0.444\text{V} \rightarrow \frac{W_9}{L_9} = \frac{2 \times 100}{120 \times 0.444^2} \approx \underline{9}$



Folded Cascode, Class B, Diff. Output Op Amp Design

Example 3 - Continued

$$8.) \frac{W_5}{L_5} = \frac{W_6}{L_6} = \frac{W_7}{L_7} = \frac{W_8}{L_8} = \frac{I_5}{K'_5[V_{DD} - I_{CMR^+} - |V_{T5}| + V_{T1}]^2} = \frac{25}{25 \times [2.5 - 2]^2} = 4$$

$$9.) \text{ Choose } I_{22} = 100\mu\text{A} \text{ and } I_{R1} = 10\mu\text{A}, \text{ therefore } P_{diss} = 2.5\text{V} \times (250\mu\text{A} + 100\mu\text{A} + 10\mu\text{A}) = 0.9\text{mW}$$

$$10.) W_{22}/L_{22} = (100\mu\text{A}/125\mu\text{A}) \times 160 = 128 \rightarrow 64\mu\text{m}/0.5\mu\text{m}$$

$$11.) \text{ Choose } GB_{cm} = 1\text{MHz} \Rightarrow 20\pi \times 10^6$$

$$\text{Therefore } \frac{W_{18}}{L_{18}} = \frac{g_m^2}{K'_1 I_{22}} = \frac{(62.8)^2}{25 \times 100} = 1.58 \rightarrow 2, \frac{W_{19A}}{L_{19A}} = \frac{W_{19B}}{L_{19B}} = 1$$

$$12.) \text{ Let } W_{20}/L_{20} = W_{21}/L_{21} = (125\mu\text{A}/50\mu\text{A}) W_{16}/L_{16} = 50$$



$$13.) R_1 = V_{OCM}/I_{R1} = 125\text{k}\Omega, R_2 = 250\text{k}\Omega - 125\text{k}\Omega = 125\text{k}\Omega$$

$$14.) \text{ Design } W\text{'s and } L\text{'s. Choose } L_{18} \text{ and } L_{19} \text{ as } 1\mu\text{m} \text{ giving } W_{18} = 1\mu\text{m} \text{ and } W_{19A} = W_{19B} = 0.5\mu\text{m. Choose } L_{20} \text{ and } L_{21} \text{ as } 1\mu\text{m} \text{ which gives } W_{20} = W_{21} = 50\mu\text{m.}$$

$$15.) \text{ Find the gain: } g_m = 200\mu\text{S}, g_{mp} = \sqrt{2 \times 25 \times 160 \times 125} = 1\text{mS},$$

$$r_{dsp} = 1/\lambda_p I_{10} = 100\text{k}\Omega, g_{mn} = \sqrt{2 \times 120 \times 20 \times 125} = 775\mu\text{S}, \text{ and } r_{dsn} =$$

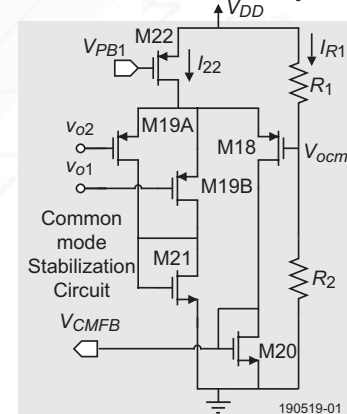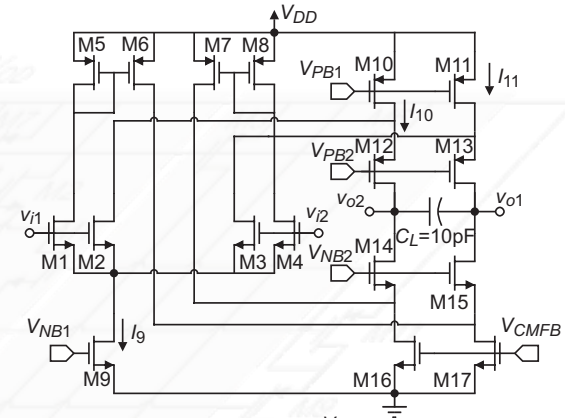
$$1/\lambda_n I_{16} = 133\text{k}\Omega \rightarrow R_L = 2 \times \left(\frac{g_{mp}}{\lambda_p^2 I^2} \parallel \frac{g_{mn}}{\lambda_n^2 I^2} \right) = 11.6\text{M}\Omega \rightarrow A_{vd} = 7,288\text{V/V}$$



CM Feedback Circuit Frequency Response

CM Feedback GB vs Differential GB:

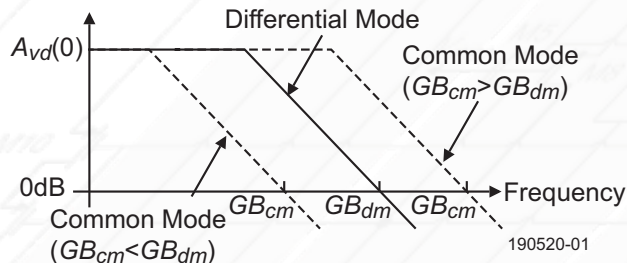Should the GB of the common mode feedback stabilization circuit (GB_{cm}) be greater or less than the GB of the differential mode (GB_{dm})?



- $GB_{dm} > GB_{cm}$ means that common mode stabilization circuit is slower than the differential mode circuit
 - Common mode stabilization does not respond to quick changes in the differential mode circuit
- $GB_{dm} < GB_{cm}$ means that common mode stabilization circuit is faster than the differential mode circuit
 - Common mode stabilization circuit can respond to fast changes in the differential mode circuit and possibly create nonlinearity in the differential mode response

Differential Output Op Amp Design

Summary:

- Differential output op amps
 - Single-ended loads
 - Differential loads
- Output common mode stabilization
- Single stage, class A, differential output op amp
 - Design Procedure OA16
 - Example 1
- Folded cascode, class A, differential output op amp
 - Design Procedure OA17
 - Example 2
- Folded cascode, class B, differential output op amp
 - Design Procedure OA18
 - Example 3