

LECTURE 1 - HOW TO DESIGN BIAS CIRCUITS INDEPENDENT OF V_{DD} AND TEMPERATURE

Topics:

- How temperature influences circuit performance
- Bias voltages independent of V_{DD} (V) and temperature (T)
- Series and parallel bias circuits
- Design procedures
- Examples

What will I learn?

- The principles of V_{DD} (V) and temperature (T) influence
- How to design voltage and current bias circuit that minimize the influence of temperature

Dr. Phillip Allen

Prof. Emeritus, ECE, Georgia Tech

Version 180730

Temperature Influence (T) on Bias Circuits

How does temperature influence circuits?

1. MOSFETs: $i_D = \frac{K'_N W}{2L} (V_{GS} - V_T)^2$

$$K'_N(T) = K'_N(T_0) \left(\frac{T}{T_0}\right)^{-1.5} \quad \text{and} \quad V_T(T) = V_T(T_0) + \alpha(T - T_0)$$

$\alpha \approx -2\text{mV}/^\circ\text{C}$ to $-3\text{mV}/^\circ\text{C}$ for NMOS (PMOS has a positive sign)

2. BJTs: $i_C = \beta I_s \exp\left(\frac{V_{BE}}{V_t}\right)$

$$\beta(T) \cong \beta(T_0) \left(\frac{T}{T_0}\right)^2, \quad I_s(T) = AT^\gamma \exp\left(\frac{-V_{BG}}{V_t}\right), \quad \text{and} \quad V_t = \frac{kT}{q}$$

A is a temperature independent constant

3. Resistors:

$$R(T) = R(T_0) + TC_1 \times (T - T_0) + TC_2 \times (T - T_0)^2 + \dots$$

4. Capacitors:

$$C(T) = C(T_0) + TC_1 \times (T - T_0) + TC_2 \times (T - T_0)^2 + \dots$$

Temperature Independent Bias Circuits

Principle

Cancel a positive going TC with a negative going TC

$$V_{REF} = V_{PTAT}(T) + K \cdot V_{CTAT}(T)$$


where

$V_{PTAT}(T)$ is a voltage that is *proportional to absolute temperature* (PTAT)

$V_{CTAT}(T)$ is a voltage that is *complimentary to absolute temperature* (CTAT)

and

 K is a temperature independent constant that makes $V_{REF}(T)$ independent of temperature




Problem – finding true PTAT and CTAT voltages!

PTAT and CTAT Voltages


PTAT and CTAT Circuits

PTAT:

 

$$V_{PTAT} = V_t \ln(N) \text{ if } I_1 = I_2$$

CTAT:

 

Nonlinear term

$$V_{CTAT} = V_{BG} - V_t(\gamma - \alpha) \ln(T) - V_t \ln\left(\frac{A}{B}\right)$$

where $I_s = AT^\gamma \exp\left(\frac{-V_{BG}}{V_t}\right)$ and $i_{PTAT} = BT^\alpha$

Temperature and V_{DD} Independent Sources

Simple Series Bias Circuit

Circuit:

$$V_{REF} = I_{PTAT}R_2 + V_{CTAT} = (R_2/R_1)V_{PTAT} + V_{CTAT} \\ = KV_{PTAT} + V_{CTAT}$$

Substituting for V_{PTAT} and V_{CTAT} gives,

$$V_{REF} = KV_t \ln(N) + V_{BG} - V_t(\gamma - \alpha) \ln(T) - V_t \ln\left(\frac{A}{B}\right)$$

Differentiating with respect to T and setting $T = T_0$ gives,

$$\frac{dV_{REF}}{dT}(T = T_0) = K \frac{V_{t0}}{T_0} \ln(N) - \frac{V_{t0}}{T_0} (\gamma - \alpha) \ln(T_0) - \frac{V_{t0}}{T_0} (\gamma - \alpha) - \frac{V_{t0}}{T_0} \ln\left(\frac{A}{B}\right)$$

Setting the derivative equal to zero, gives,


$$K \ln(N) - \ln\left(\frac{A}{B}\right) = (\gamma - \alpha)[1 + \ln(T_0)]$$

Substituting back gives,

$$V_{REF} = (\gamma - \alpha)V_t[1 + \ln(T_0)] + V_{BG} - V_t(\gamma - \alpha) \ln(T) = V_{BG} + (\gamma - \alpha)V_t \left[1 + \ln\left(\frac{T_0}{T}\right)\right]$$

At $T = T_0$, the reference voltage is
 
$$V_{REF} = V_{BG} - V_t(\gamma - \alpha) = 1.205V + 0.057V = 1.262V \quad (T = T_0 = 27^\circ\text{C})$$



Design Procedure BT1

The diagram shows a PTAT current source circuit. It consists of three PMOS transistors (M1, M2, M3) and two NMOS transistors (Q1, Q2). M1 and Q1 are connected in a diode configuration with current I_1 . M2 and Q2 are connected in a diode configuration with current I_{PTAT} . M3 and Q3 are connected in a diode configuration with current I_{PTAT} . The gates of M1, M2, and M3 are connected to V_{DD} . The gates of Q1 and Q2 are connected to a common node. The gates of Q3 and Q4 are connected to a common node. The sources of M1, M2, and M3 are connected to V_{DD} . The sources of Q1, Q2, and Q3 are connected to a common node. The source of Q4 is connected to ground. The output voltage V_{REF} is taken from the node between M3 and Q3. The circuit is labeled with 180423-04.

$$V_{REF} = \frac{R_2}{R_1} V_{PTAT} + V_{CTAT}$$




Use Example 1 of Bias Design Independent of V_{DD} and Process to design a series reference voltage.

$$2.) R_2/R_1 = -[(-2000\mu V/^{\circ}C)/(200\mu V/^{\circ}C)] = 10 \rightarrow R_2 = 10 \times 29.93k\Omega = 299.3k\Omega$$

^{††} See how to design startup circuits


Temperature and V_{DD} Independent Sources

   Tuning the Simple Temperature Independent Bias Circuit



Brokaw Bandgap

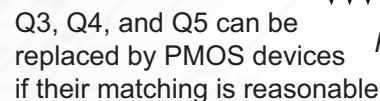Simple Bandgap Bandgap ($V_{REF} > V_{BG}$) Improved PSR Bandgap



Temperature and V_{DD} Independent Sources

Brokaw Design Procedure BT2

Step	Design Equations	Comments
Simple Brokaw Bandgap, $V_{REF} = V_{BG}$		
1	$R_2 = V_T \ln(N) / I_{PTAT}$	Choose I_{PTAT} , N = Area of Q2/Area of Q1
2	$R_1 = \frac{R_2 T (dV_{BE1} / dT)}{2 V_T \ln(N)} = \frac{R_2 \cdot 300 (\approx 2mV / ^\circ C)}{2 \cdot 0.0258 \ln(N)}$	Makes $dV_{BG}/dT \approx 0$, need a good value for $ dV_{BE1}/dT $ or use $2mV/^\circ C$
Brokaw Bandgap with $V_{REF} > V_{BG}$		
3	$R_4 + R_5 = \frac{V_{REF}}{I_{4,5}}$	Choose the current through R_4 and R_5 , $I_{4,5}$. V_{REF} is the output greater than V_{BG} .
4	$R_5 = \frac{V_{BG}}{V_{REF}} (R_4 + R_5)$ and $R_4 = (R_4 + R_5) - R_5$	Designs the increase of V_{BG} to V_{REF}
5	$R_3 = \frac{R_2 R_4 R_5}{R_1 (R_4 + R_5)}$	Eliminates the base currents of Q1 and Q2
Brokaw Bandgap with improved PSR (PTAT circuit)		
6	$R_6 = V_T \ln(N) / I_{PTAT}$	Choose I_{PTAT} , N = Area of Q2/Area of Q1
7	Choose W/L of M1 and M2, $M3 = 4 \times M2$	Cancels base current of Q3, Q4, and Q5
8	Q3 = Q4 = Q5, M6 arbitrary	

Temperature and V_{DD} Independent Sources

Example 2 – Brokaw BG Design

Let $V_{DD} = 5V$ and $I_{Supply} \leq 10\mu A$. Design $V_{REF} = 1.5V$

1.) Let $N=8$ & choose $I_{PTAT} = 2\mu A$, therefore

$$R_2 = \frac{V_t \ln(8)}{I_{PTAT}} = 26.83k\Omega$$

2.) Design R_1 , $R_1 = \frac{R_2 T (dV_{BE}/dT)}{2V_t \ln(N)} = \frac{26.83k\Omega \times 300K (2mV/^{\circ}C)}{2 \times 0.0258 \times 2.079}$
 $= 150k\Omega$

3.) Let $I_{4,5} = 2\mu A$, then $R_4 + R_5 = 1.5V / 2\mu A = 750k\Omega$


4.) $R_5 = \frac{V_{BG}}{V_{REF}} (R_4 + R_5) = \left(\frac{1.262}{1.5} \right) (750k\Omega) = 631k\Omega$. $R_4 = 750k\Omega - 631k\Omega = 119k\Omega$

5.) $R_3 = (R_2 R_4 R_5) / [R_1 (R_4 + R_5)] = (26.83k \cdot 119k \cdot 631k) / [150k (750k)] = 4.475k\Omega$

6.) $R_6 = V_t \ln(N) / I_{PTAT} = 0.0258 \cdot 2.079 / 2\mu A = 26.82k\Omega$

7.) Choose $W_1/L_1 = W_2/L_2 = 20\mu m / 10\mu m$ and $W_3/L_3 = 80\mu m / 10\mu m$

 8.) Let the emitter area of Q1, Q3, and Q4 be $10\mu m^2$, Q2 is $x10Q1$, Q5 is $2xQ1$, and $W_6/L_6 = 40\mu m / 1\mu m$.




Temperature and V_{DD} Independent Sources


Parallel Bandgap

Combine I_{PTAT} with I_{CTAT} to yield a reference voltage.

I_{CTAT} circuit:

 

Parallel Bandgap Circuit:

 


$$V_{REF} = R_3(I_{PTAT} + I_{CTAT}) = R_3 \left(\frac{V_{PTAT}}{R_1} + \frac{V_{CTAT}}{R_2} \right) = \frac{R_3}{R_2} \left(\frac{R_2}{R_1} V_{PTAT} + V_{CTAT} \right)$$

Temperature and V_{DD} Independent Sources

Parallel Design Procedure BT3

Step	Design Equations	Comments
1	Select $I_1, I_2, I_3, I_4, I_5, I_6$, and I_7	$P_{diss} = V_{DD} (\sum_{i=1}^7 I_i)$
2	Use Design Procedure BT1 to design Q1, Q2, M1, M2 and R_1 .	
3	Let M4 and M7 equal M2.	I_{PTAT} currents equal
4	Let M3=M5=M6=M2, $W_8/L_8 = 10\mu\text{m}/2\mu\text{m}$, and Q3=Q1	Design of M8 is arbitrary
5	$R_2/R_1 = -\left(\frac{dV_{CTAT}/dT}{dV_{PTAT}/dT}\right) = -\left(\frac{dV_{CTAT}/dT}{200\mu\text{V}/^\circ\text{C}}\right)$	$\frac{dV_{CTAT}}{dT} \approx -2\text{mV}/^\circ\text{C}$
6	$R_3 = V_{REF} R_2 \left(\frac{R_2}{R_1} V_{PTAT} + V_{CTAT}\right)^{-1}$	V_{REF} specified

 

Example 3

Design a parallel voltage reference of 0.75V. $V_{DD}=5\text{V}$, and $I_{\text{Supply}} 15\mu\text{A}$.
1.) Select all currents as $2\mu\text{A}$.

2.) From BT1, the W/L of M1, M2, M3, M4, M5, M6, and M7 = $50\mu\text{m}/10\mu\text{m}$, the area of Q1 is $10\mu\text{m}^2$ and Q2 = $100\mu\text{m}^2$, $R_1=29.93\text{k}\Omega$ and $R_2 = 10 \times 29.93\text{k}\Omega = 299.3\text{k}\Omega$.

3.) $W_8/L_8=10\mu\text{m}/2\mu\text{m}$ and $R_3=V_{REF} R_2 \left(\frac{R_2}{R_1} V_{PTAT} + V_{CTAT}\right)^{-1} = (0.75 \times 299.3\text{k}) / 1.262 = 177.9\text{k}\Omega$

Troubleshooting Bandgap Designs

Debugging Advice


90% of the issues having to do with the bandgap not working properly have to do with how well the current mirror performs as temperature, V_{DD} or process changes.

If you are having problems, simulate currents in the current mirror and check to see that they track.

This is what they should look like:

If the currents in the current do not track, consider improving the matching of the current mirror by cascading or other means of improving the matching.

 Be careful at high temperatures of leakage currents influencing the bandgap design.



Summary – Bandgap Design

Voltage and Temperature Independent Bias Design

- Objective of biasing – independence of V_{DD} and temperature
- Principle is to cancel a positive going voltage with respect to temperature with a negative going voltage
- Simple bandgap
- Brokaw bandgap
- Parallel bandgap
- Design procedures – BT1, BT2, and BT3
- Examples
- Troubleshooting bandgap designs