

LECTURE 4 - HOW TO DESIGN ULTRA-STABLE TEMPERATURE INDEPENDENT BIAS CIRCUITS

Topics:

- Temperature stable bias currents
- Issues with ultra-precision bandgap references
- Curvature corrected bandgap with V_{DD} independence
- Design procedure
- Trimming and influence of process

What will I learn?

- How to design temperature independent voltage sources with a temperature coefficient of 1ppm/°C or less over -50°C to 125°C.

Dr. Phillip Allen



Prof. Emeritus, ECE, Georgia Tech

Version 190802

Temperature Stable Bias Currents

Principle

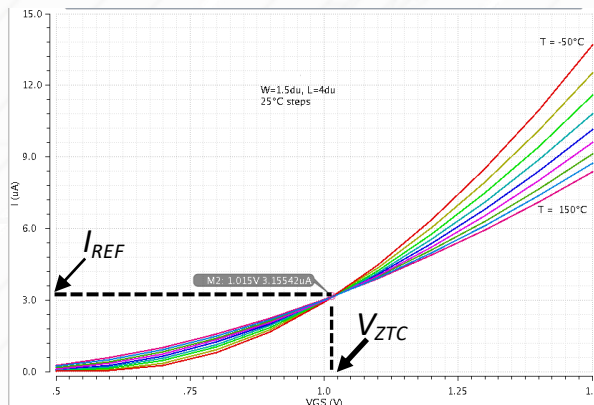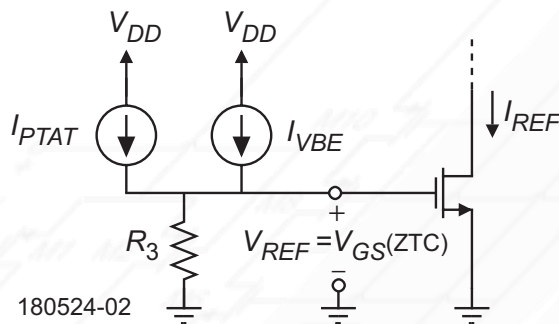Use a MOSFET in ZTC operation and design the parallel form of the bandgap voltage reference equal to the value of V_{ZTC} .



Comments

- Ability of the ZTC point not to drift with temperature will restrict the temperature range
- The reference voltage must be equal to the ZTC voltage
- The voltage V_{REF} will suffer the bandgap curvature problem which will be translated onto I_{REF} .

PTAT and CTAT Voltages

Bandgap Curvature

PTAT is perfectly linear with respect to T


$$V_{PTAT} = V_t \ln(N) \text{ if } I_1 = I_2$$

CTAT has a term that is not linear with respect to T that causes the bandgap curvature.

$$V_{CTAT} = V_{BG} - V_t(\gamma - \alpha) \ln(T) - V_t \ln\left(\frac{A}{B}\right)$$

$$\text{where } I_s = AT^\gamma \exp\left(\frac{-V_{BG}}{V_t}\right) \text{ and } i_{PTAT} = BT^\alpha$$

Result of adding V_{PTAT} to V_{CTAT} :

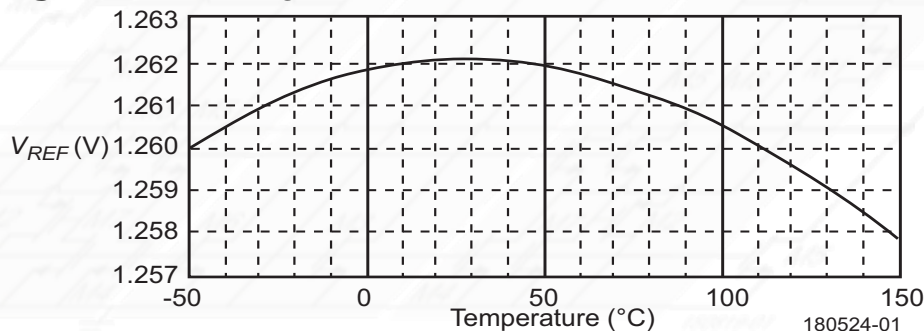

Cancellation of Nonlinear CTAT Term

Principle:

Eliminate the nonlinear term of the following CTAT expression:

$$V_{CTAT}(\alpha) = V_{BG} - (\gamma - \alpha)V_t \ln(T) - V_t \ln(A/B)$$

Generate the following:

$$V_{CTAT}(\alpha = 1) = V_{BG} - (\gamma - 1)V_t \ln(T) - V_t \ln(A/B) \rightarrow I_{CTAT}'(\alpha=1) = V_{CTAT}(\alpha=1)/R_2$$

and

$$V_{CTAT}(\alpha = 0) = V_{BG} - \gamma \ln(T) - V_t \ln(A/B) \rightarrow I_{CTAT}'(\alpha=0) = V_{CTAT}(\alpha=0)/R_4$$

Combine the psuedo PTAT and 2 CTAT currents as follows,

$$V_{REF} = K_1 \cdot I_{PTAT}' + K_2 \cdot I_{CTAT}'(\alpha=1) - K_3 \cdot I_{CTAT}'(\alpha=0)$$

and


$$V_{REF} = \frac{R_3}{R_1} V_{PTAT} + \frac{R_3}{R_2} V_{CTAT}(\alpha = 1) - \frac{R_3}{R_4} V_{CTAT}(\alpha = 0)$$

To cancel the nonlinear terms requires that:

$$(R_3/R_2)(\gamma - 1)V_t \ln(T) = (R_3/R_4)\gamma V_t \ln(T) \text{ or } R_4/R_2 = \gamma/(\gamma - 1)$$

Therefore we can write,
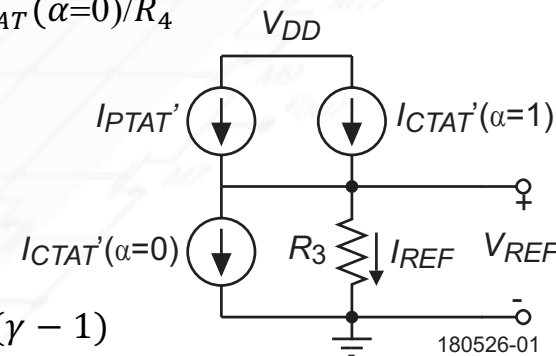
$$V_{REF} = (R_3/R_1)V_{PTAT} + (R_3/\gamma R_2)V_{CTAT} \text{ where } V_{CTAT} = V_{BG} - V_t \ln(A/B)$$



Ultra-Stable Temperature Reference

Design Equations

From last slide,

$$V_{REF} = (R_3/R_1)V_{PTAT} + (R_3/\gamma R_2)V_{CTAT} \quad \text{where } V_{CTAT} = V_{BG} - V_t \ln(A/B)$$

Differentiate with respect to temperature to get,

$$\frac{dV_{REF}}{dT} = \frac{R_3}{R_1} \frac{V_{PTAT}}{T} + \frac{R_3}{\gamma R_2} \frac{dV_{CTAT}}{dT} = 0 \Rightarrow \frac{R_2}{R_1} = \frac{-T(dV_{CTAT}/dT)}{\gamma \times V_{PTAT}}$$

Substituting back into V_{REF} gives,

$$V_{REF} = \frac{R_3}{\gamma \times R_2} \left[\frac{\gamma R_2}{R_1} V_{PTAT} + V_{CTAT} \right] = \frac{R_3}{\gamma \times R_2} \left[-T \frac{dV_{CTAT}}{dT} + V_{CTAT} \right]$$

But,

$$\frac{dV_{CTAT}}{dT} = -\frac{V_t}{T} \ln(A/B) \rightarrow V_{REF} = \frac{R_3}{\gamma \times R_2} [V_t \ln(A/B) + V_{BG} - V_t \ln(A/B)] = \frac{R_3}{\gamma \times R_2} V_{BG}$$

The design equations are:

- 1.) $R_1 = V_{PTAT}/I_{PTAT}$
- 2.) $R_2 = [-T(dV_{CTAT}/dT)/\gamma \times V_{PTAT}]R_1 \approx [T(2mV/^{\circ}C)/\gamma \times V_{PTAT}]R_1$
- 3.) $R_4 = (\gamma/\gamma - 1)R_2$
- 4.) $R_3 = [\gamma \times V_{REF}/V_{BG}] R_2$

PTAT Linearity Issues

Problem with canceling the nonlinear term

In order for the previous principle to work, V_{PTAT} must be linear with temperature.

Consider the following model for a BJT:

$$\begin{aligned} V_{PTAT} &= V_1 - V_2 = V_{BE1} + R_{B1}I_{B1} - V_{BE2} + R_{B2}I_{B2} \\ &= V_t \ln\left(\frac{I_1}{I_{S1}}\right) + R_{B1}I_{B1} - V_t \ln\left(\frac{I_2}{I_{S2}}\right) - R_{B2}I_{B2} \end{aligned}$$

Assume $I_1 = I_2$ and $I_{B1} = I_{B2}$ gives,

$$V_{PTAT} = V_t \ln(N) + I_{B1}(R_{B1} - R_{B2})$$

But $R_B \propto 1/N \times A$ where A is the area of the emitter.


Therefore, since $R_{B1} = N \times R_{B2}$,

$$V_{PTAT} \propto V_t \ln(N) + \frac{I_B R_B}{A} \left(1 - \frac{1}{N}\right)$$

To linearize V_{PTAT} we must make A large, I_B small, and $N \approx 1$

However, as A becomes large, the leakage current at high temperatures causes V_{PTAT} to be nonlinear.

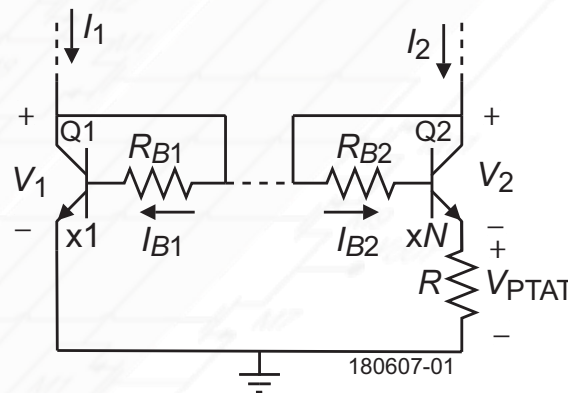To cancel the nonlinear term, I should be less than $1\mu\text{A}$, $N \approx 2-6$, and emitter area as large as possible without experiencing high temperature leakage.



Configuration Issues

Preserving I_{PTAT}

I_{PTAT} generated in the resistor R_{PTAT} must be the same I_{PTAT} (I_{PTATX}) going to the upper current mirror.

- For base-connected PTAT circuit,
- For base-disconnected PTAT circuit,



$$I_{PTATX} = I_C = \alpha \times I_E = \alpha \times I_{PTAT}$$

$$I_{PTATX} = I_C + I_B = I_E = I_{PTAT}$$

Result:

Temperature influence of α causes $I_{PTAT} - I_{PTATX}$ to vary over temperature for base-connected PTAT circuits.

Unfortunately, techniques other than op amps do not achieve sufficient reduction of $|I_{PTAT} - I_{PTATX}|$.

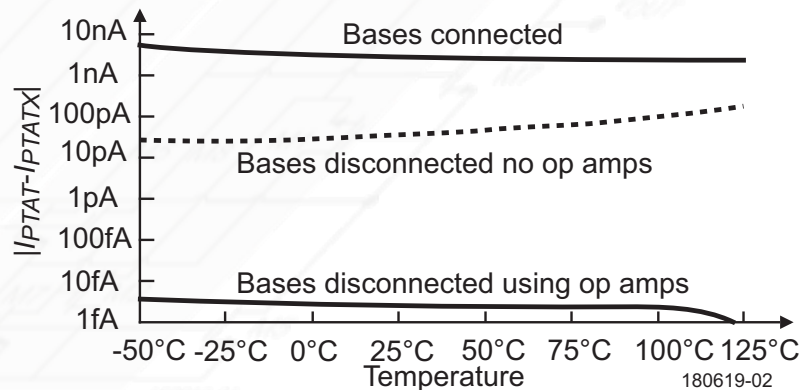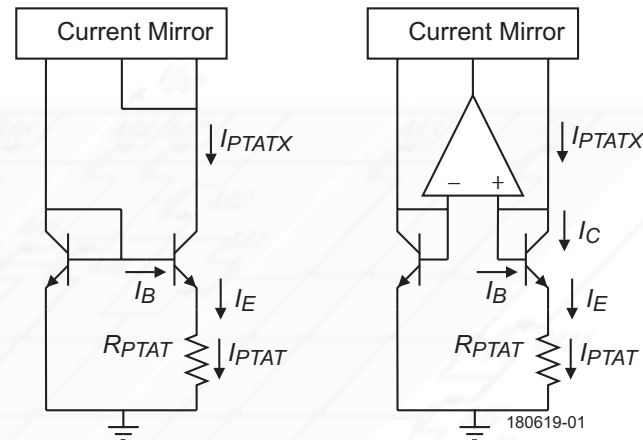

Configuration Issues - Continued

Preserving I_{CTAT}

I_{CTAT} generated in the resistor R_{PTAT} must be the same I_{PTAT} (I_{CTATX}) going to the upper current mirror.

- For base-connected CTAT circuit,

$$I_{CTATX} = I_B + I_{CTAT}$$



- For base-disconnected CTAT circuit,

$$I_{PTATX} = I_{PTAT}$$

Result:


Temperature influence of α causes $I_{CTAT} - I_{CTATX}$ to vary over temperature for base-connected CTAT circuits.

Unfortunately, techniques other than op amps do not achieve sufficient reduction of $|I_{CTAT} - I_{CTATX}|$.

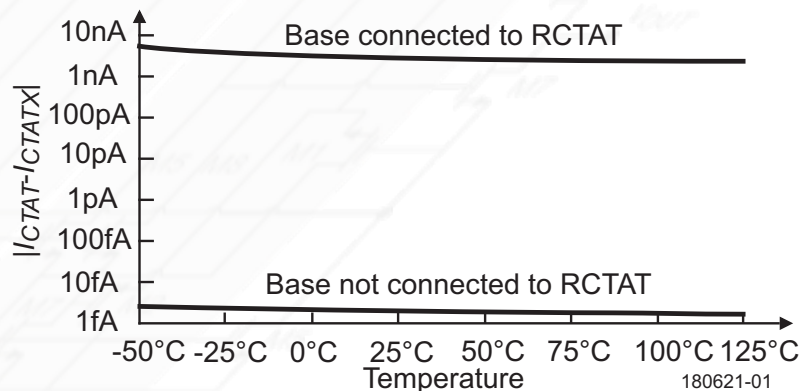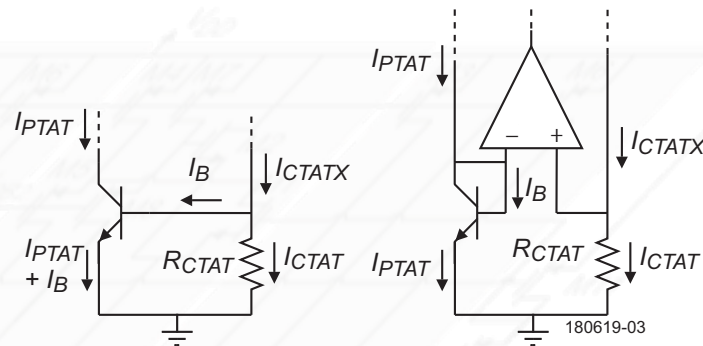

Temperature and V_{DD} Independent Sources

Circuit Implementation:

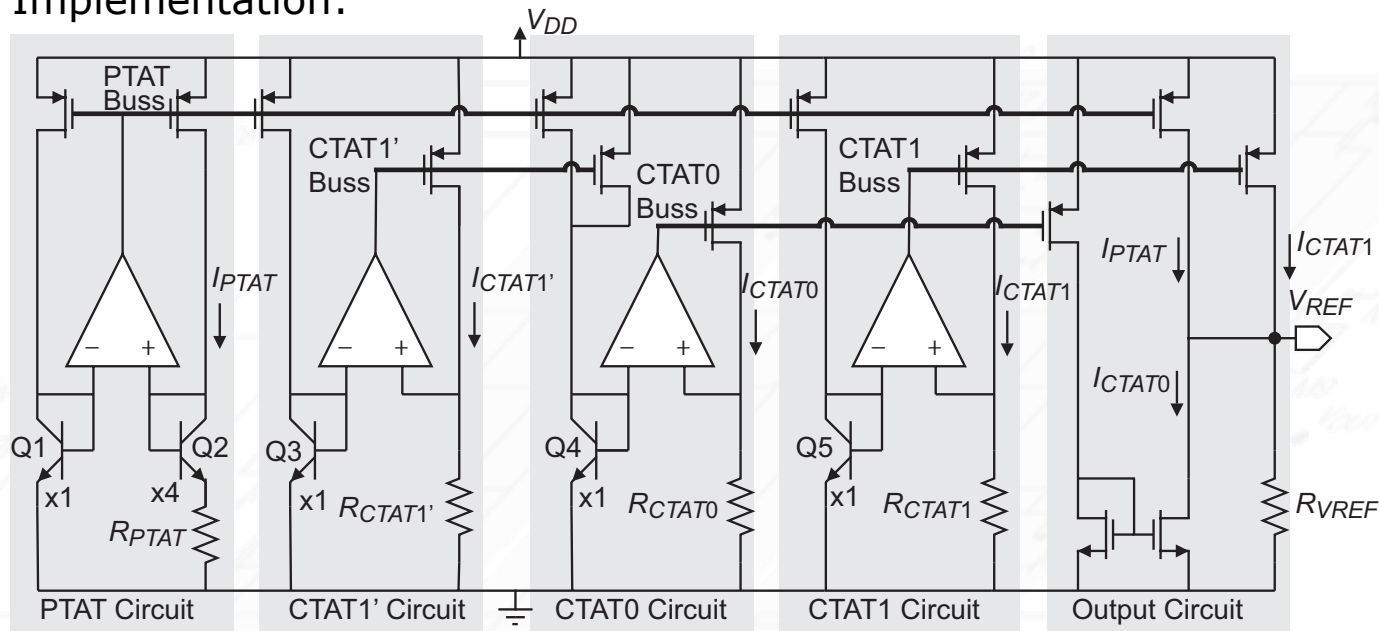

180621-02

Note that two CTAT1 generators are necessary-


1. One is used to generate CTAT0 (CTAT1')
2. One is used to create V_{REF} (CTAT1)
3. Cannot cancel the nonlinear term if changing CTAT1 influences CTAT0

Op Amps?

Requirements

- Gain $\geq 60\text{dB}$
- $\geq 45^\circ$ phase margin
- Minimize the input offset voltage (should be less than 10 times the anticipated ΔV_{REF})

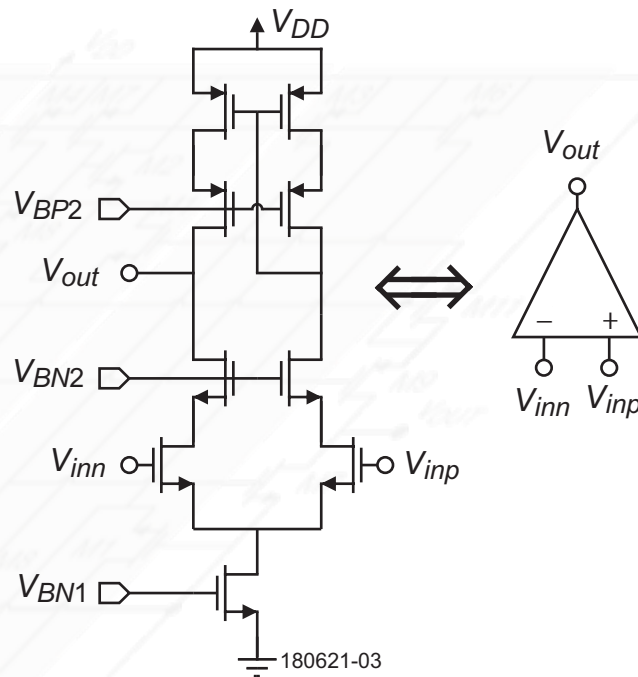The op amps used in the curvature corrected bandgap design need only be one-stage because the current mirror and resistive load constitute a second stage.



For details on the design of the op amp see *How to Design Op Amps* in the *How to Design Analog IC Circuits Series*.

Ultra-Stable Temperature and V_{DD} Independent Source Design

Ultra-Stable Design Procedure BT4

Step	Design Equations	Comments
1	$R_{PTAT} = 1.386V_t/I_{PTAT}$	Choose $I_{PTAT} \leq 1\mu A$, N = Area of Q2/Area of Q1 = 4
2	$R_{CTAT1'} = (R_{PTAT}T(dV_{BE}/dT))/(V_t \ln 4)$	Makes $dI_{CTAT0}/dT \approx 0$, need a good value for $ dV_{BE}/dT $ or use $2mV/^{\circ}C$.
3	$R_{CTAT1} = \frac{R_{PTAT}T(dV_{BE}/dT)}{\gamma V_t \ln(4)}$	Makes $dV_{REF}/dT \approx 0$, need a good value for $ dV_{BE}/dT $ or use $2mV/^{\circ}C$. Guess $\gamma \approx 2$ if not know and adjust later
4	$R_{CTAT0} = \gamma/(\gamma - 1)R_{PTAT}$	If γ is not known guess $\gamma \approx 2$ and adjust later
5	$R_{VREF} = \frac{\gamma V_{REF}}{V_{BG}} R_{CTAT1}$	$V_{BG} \approx 1.205V$

Example 1

Let $V_{DD} = 3V$. Design $V_{REF} = 1.0V$

1.) Let $N = 4$ and choose $I_{PTAT} = 0.25\mu A$, therefore $R_2 = 1.386 \times 0.0259 / 2\mu A = 143.6k\Omega$

2.) Design $R_{CTAT1'} = R_{PTAT}T(dV_{BE}/dT)/(V_t \ln(4)) = 143.6k\Omega \times 300^{\circ}K(2mV/^{\circ}C)/(0.0258 \times 1.386) = 2.4M\Omega$

3.) Design $R_{CTAT1} = R_{PTAT}T(dV_{BE}/dT)/(\gamma V_t \ln(4)) = 143.5k\Omega \times 300^{\circ}K(2mV/^{\circ}C)/(2 \times 0.0258 \times 1.386) = 1.2M\Omega$

4.) Design $R_{CTAT0} = \gamma/(\gamma - 1)R_{CTAT1} = (2/1) \times 1.2M\Omega = 2.4M\Omega$



5.) Design $R_{VREF} = [\gamma \times V_{REF}/V_{BG}] R_{CTAT1} = (1 \times 2 \times 1.2M\Omega)/(1.205) = 2M\Omega$

Ultra-Stable Temperature and V_{DD} Independent Sources

Design adjustment Procedure

Step	Adjustment
1	Adjust R_{CTAT1} to make I_{CTAT0} flat with respect to temperature (do not change R_{PTAT} in design step 1)
2	Adjust R_{CTAT1} to make V_{REF} flat as possible with respect to temperature (do not change R_{PTAT} in design step 1)
3	Select R_{CTAT0} that is less than that in design step 4 and repeat steps 1 and 2 above.
4	Select R_{CTAT0} that is greater than that in design step 4 and repeat steps 1 and 2 above.
5	Pick the value of R_{CTAT0} that gives minimum dV_{REF}/dT or TC

Design results

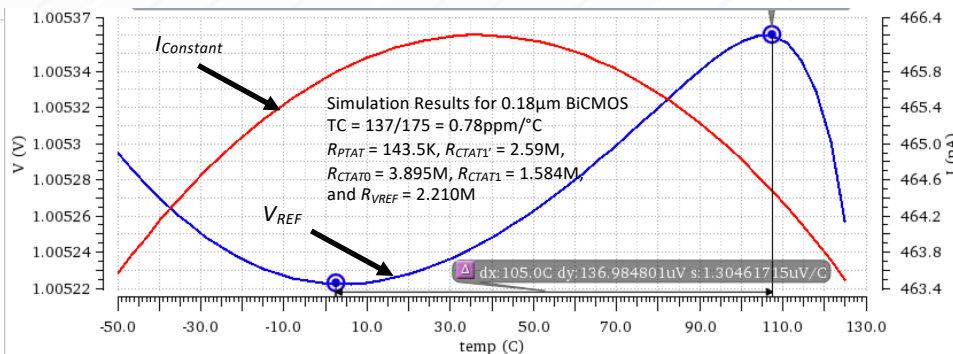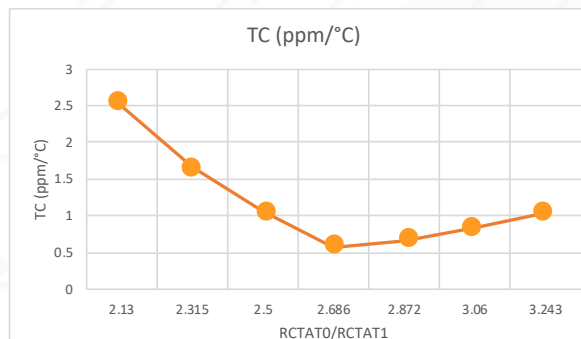

Process Dependence


Influence of Process

Unfortunately, the ultra-stable temperature reference is very sensitive to process. Tuning will be necessary in a manufacturing environment.

Trimming Procedure

1. Assume nominal meets specs
2. Trim R_{CTAT0} to make I_{CTAT0} constant
3. Trim R_{CTAT1} and R_{VREF} to achieve desired TC

Example: 

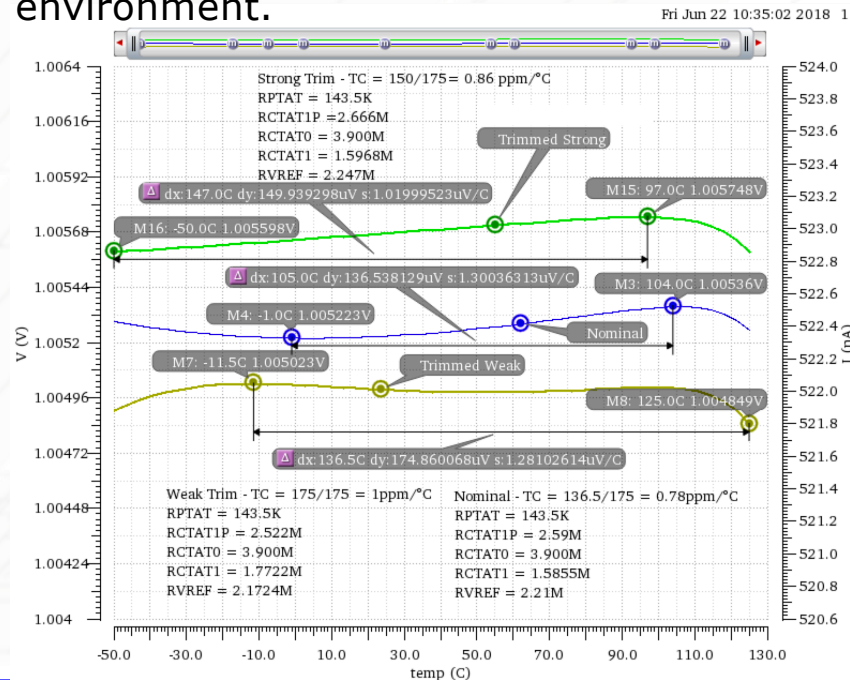

Summary – Ultra-stable temperature sources

Curvature-Corrected Bandgap Design

- How to create a temperature stable current from a temperature stable voltage
- CTAT curvature cancellation technique
- Issues with ultra-stable temperature sources
 - Base currents
 - Op amps versus no op amps
- Design procedures – BT4
- Example
- Influence of process and the need for trimming