

LECTURE 1 - HOW TO DESIGN OPEN LOOP COMPARATORS

Topics:

- Comparator characterization
- Types of comparators
- Design of single-stage comparators
- Design of folded cascode comparators
- Design of two-stage comparators

What will I learn?

- How to design open loop comparators to satisfy a given set of specifications

Dr. Phillip Allen


Prof. Emeritus, ECE, Georgia Tech

Version 200422


Characterization of Comparators

What is a Comparator?

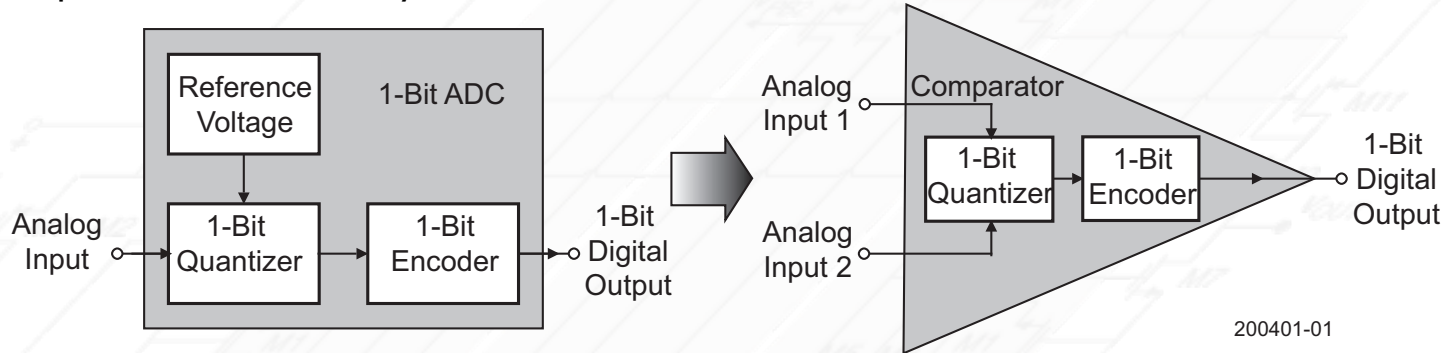- The comparator is a circuit that compares one analog signal with another analog signal or a reference voltage and outputs a binary signal based on the comparison
- The comparator is basically a 1-bit ADC



Comparator symbol:

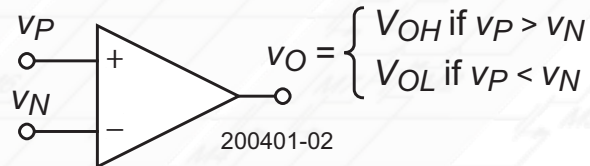

Characterization of Comparators

Characterization

The input to the comparator is analog and the characterization is essentially the same as an op amp:

- Common mode input range
- Input offset voltage
- Noise – transition uncertainty


The transfer characterization:

$$|A_V| = \frac{V_{OH} - V_{OL}}{V_{IH} - V_{IL}}$$

Output characterization:

- V_{OH} and V_{OL}
- Slew rate
- Propagation delay time

$$t_p = \frac{t_{pr} + t_{pf}}{2}$$

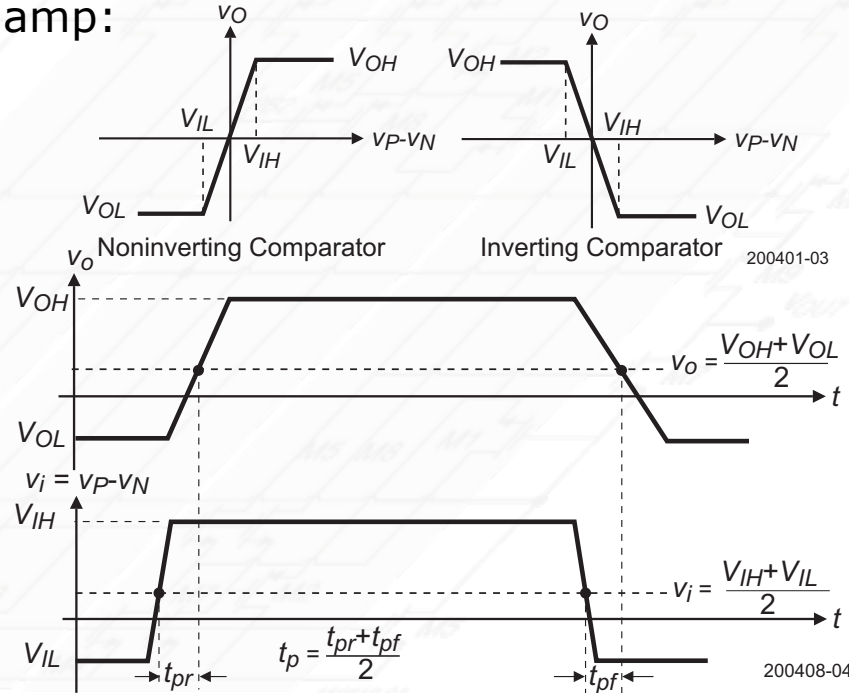

Characterization of Comparators

Propagation delay time:

Assume the gain of the comparator is $A_v(s) = \frac{A_v(0)}{s/\omega_c + 1} = \frac{A_v(0)}{s\tau_c + 1}$

The step response is $v_o(t) = A_v(0)[1 - e^{-t/\tau_c}]V_{in}$ where V_{in} is the magnitude of the step input.

The maximum slope occurs at $t = 0$ and is $\left. \frac{dv_o(t)}{dt} \right|_{t=0} = \frac{A_v(0)}{\tau_c} V_{in}$

The rising propagation time, t_{pr} , is found as,



$$\frac{V_{OH} - V_{OL}}{2} = A_v(0)[1 - e^{-t_{pr}/\tau_c}]V_{in} \rightarrow t_{pr} = \tau_c \ln \left[\frac{1}{1 - \frac{V_{OH} - V_{OL}}{2A_v(0)V_{in}}} \right] = \tau_c \ln \left[\frac{1}{1 - \frac{V_{in(min)}}{2V_{in}}} \right]$$

Define k as the ratio of V_{in} to the minimum input voltage, $V_{in(min)}$,

$$k = \frac{V_{in}}{V_{in(min)}} \rightarrow t_p = t_{pr} = \tau_c \ln \left[\frac{2k}{2k-1} \right]$$


If $k=1$, $t_p = 0.693\tau_c$

If $k=10$, $t_p = 0.051\tau_c$

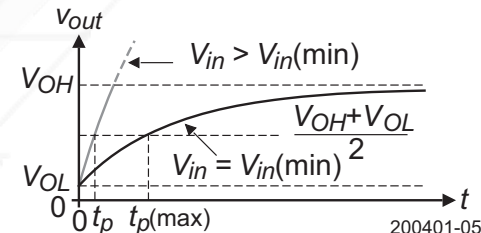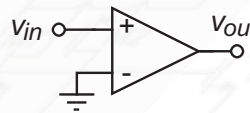


Open-Loop Comparators


Possible open-loop comparators:

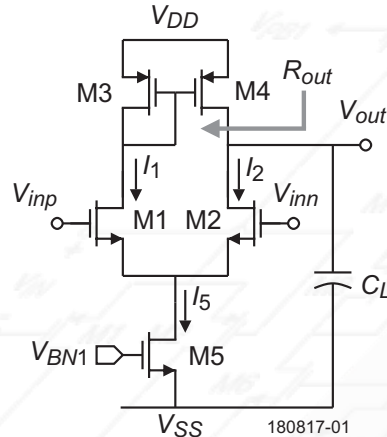

Design Procedure CO-1

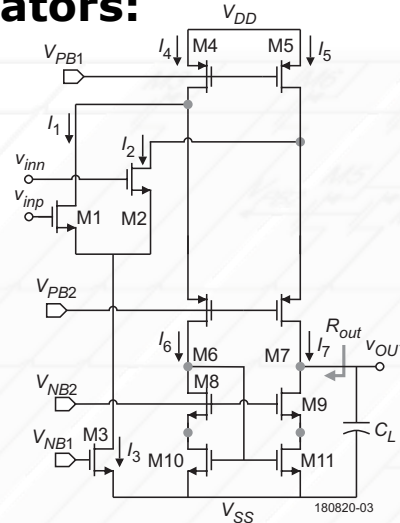

Design Procedure CO-2

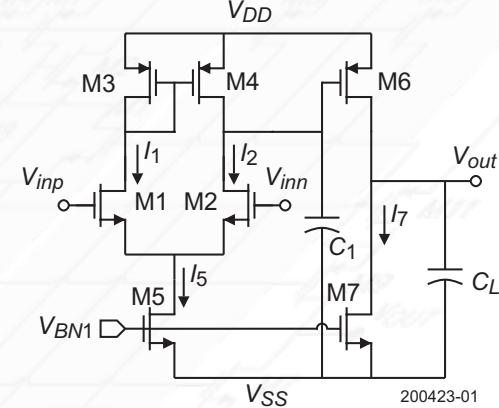

Design Procedure CO-3

Key Specifications:

- Minimum input voltage - $V_{in(min)} \Rightarrow A_v(0)$
- Propagation time delay - $t_p \Rightarrow GB$
- Slew Rate - $SR \Rightarrow I_{Sink/Source}$

Open-Loop Comparators

Slewing versus Linear Response

When does slew occur?

- Slewing occurs when the current in a capacitor becomes limited.

$$i = C \frac{dv}{dt} \rightarrow SR = \frac{dv}{dt} = \frac{i}{C}$$

- In a CMOS comparator, the input voltage must be large enough to cause the sinking/sourcing current to be on one or the other side of the differential amplifier input so that the current becomes constant.

- The value of V_{in} for this to occur is,
$$V_{in}(slew) \geq 2 \sqrt{\frac{I_{Sink/Source}}{\frac{K'}{W/L}}}$$

- This is generally much larger than the V_{in} for comparators and therefore most comparators will operate in the linear mode.
- If the comparator slews, the propagation delay time is given by,


$$t_p = \Delta T = \frac{\Delta V}{SR} = \frac{V_{OH} - V_{OL}}{2 \cdot SR}$$

where SR is the slew rate of the comparator.

Simple One-Stage Comparator Design

Design Procedure – CO1:

Step	Design Equations	Comments
This design procedure assumes $V_{in} = V_{in}(\min)$		
1	$A_v(0) = (V_{OH} - V_{OL}) / V_{in}(\min)$	V_{OH} , V_{OL} , $V_{in}(\min)$ given
2	$\frac{g_{m1}}{C_L} = GB = \frac{A_v(0)}{\tau_c} = \frac{0.693A_v(0)}{t_p} \Rightarrow g_{m1} = \frac{0.693A_v(0)}{t_p} C_L$	Assumes t_p and C_L are given.
3	$\frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{g_{m1}^2}{K'_N I_5}$	Choose I_5
4	$\frac{W_3}{L_3} = \frac{W_4}{L_4} = \frac{I_5}{K'_3 [V_{DD} - ICMR^+ - V_{T3} + V_{T1}]^2}$	$ICMR^+ = V_{in}(\max)$ specified, $M3 = M4$
5	$\frac{W_5}{L_5} = \frac{2I_5}{K'_N (ICMR^- - V_{GS1})^2}$, $V_{GS1} = \sqrt{I_5 / K'_N \left(\frac{W_1}{L_1} \right)} + V_{T1}$	Note that $ICMR^-$ must be greater than V_{GS1}
6	Check power dissipation, $P_{diss} = V_{DD} I_5$	Change I_5 in step 3 to meet power dissipation

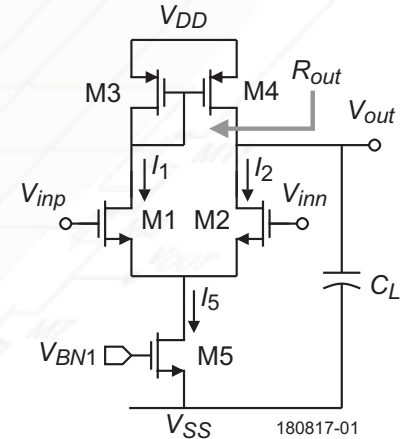


Example 1

$t_p = 10 \mu s$	$V_{DD} = 2.5V$	$V_{OH} = 2V$	$V_{OL} = 0.5V$	$V_{in}(\min) = 10mV$	$1V \leq ICMR \leq 2V$
------------------	-----------------	---------------	-----------------	-----------------------	------------------------

$$2.) g_{m1} = \frac{0.693A_v(0)}{t_p} C_L = \frac{0.693 \times 150 \times 10 pF}{10 \mu s} = 104 \mu S$$

$$4.) \frac{W_3}{L_3} = \frac{W_4}{L_4} = \frac{I_5}{K' I_3 [V_{DD} - I_{CMR}^+ - |V_{T3}| + V_{T1}]^2} = \frac{10 \times 10^{-6}}{25 \times 10^{-6} [2.5 - 2]^2} = 1.6 \rightarrow 2$$

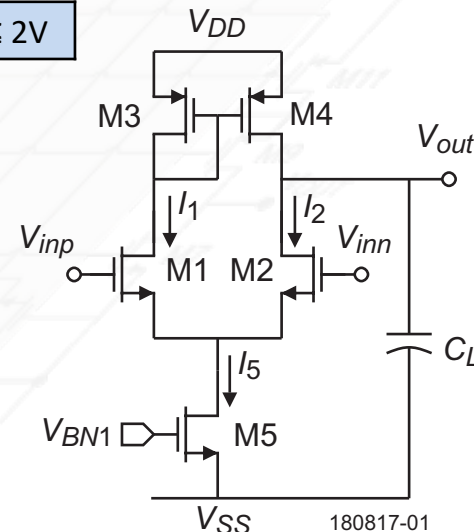
$$\frac{W_5}{L_5} = \frac{2I_5}{K'_N(ICMR^- - V_{GS1})^2} = \frac{20}{120(1-0.596)^2} = 1$$



Folded Cascode Comparator Design

Design Procedure – CO2

Step	Design Equations	Comments
This design procedure assumes $V_{in} = V_{in}(\min)$		
1	$A_v(0) = (V_{OH} - V_{OL}) / V_{in}(\min)$	V_{OH} , V_{OL} , $V_{in}(\min)$ given
2	$g_{m1} = \frac{0.693 A_v(0)}{t_p} C_L$	Assumes t_p and C_L are given.
3	$\frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{g_{m1}^2}{2K'_N I_3}$	Choose I_3 and I_4 and I_5
4	$\frac{W_3}{L_3} = \frac{2I_3}{K'_N (ICMR^- - V_{GS1})^2}$, $V_{GS1} = \sqrt{\frac{I_3}{K'_N (\frac{W_1}{L_1})}} + V_{T1}$	Note that $ICMR^-$ must be greater than V_{GS1}
5	$W_4/L_4 = W_5/L_5 = 4I_4/[K'_P(V_{DD} - V_{OH})^2]$	$V_{SD4}(\text{sat}) = 0.5[V_{DD} - V_{OH}]$
6	$W_6/L_6 = W_7/L_7 = 4I_6/[K'_P(V_{DD} - V_{OH})^2]$	$V_{SD6}(\text{sat}) = 0.5[V_{DD} - V_{OH}]$
7	$\frac{W_8}{L_8} = \frac{W_9}{L_9} = \frac{W_{10}}{L_{10}} = \frac{W_{11}}{L_{11}} = \frac{4I_6}{K'_N V_{OL}^2}$	$V_{DS8}(\text{sat}) = 0.5[V_{OL} - V_{SS}]$
8	$P_{diss} = V_{DD}(I_4 + I_5)$	Can change currents if too large

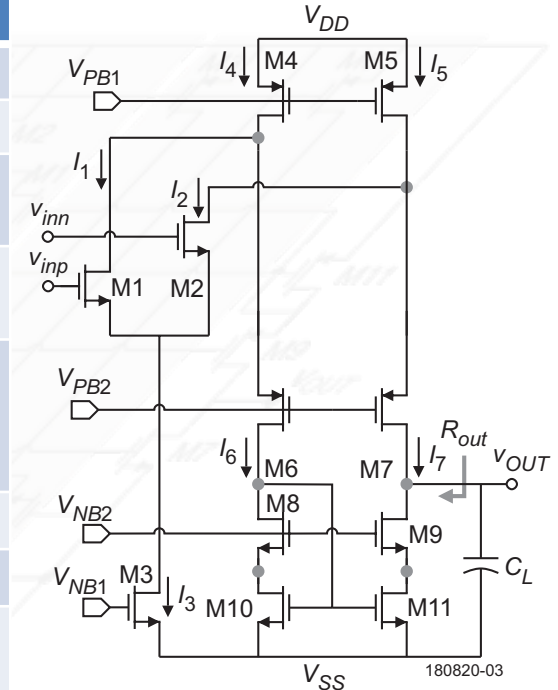


Folded Cascode Comparator Design

Example 2

If $K_N' = 120\mu\text{A}/\text{V}^2$, $K_P' = 25\mu\text{A}/\text{V}^2$, $V_{TN} = |V_{TP}| = 0.5\text{V}$, $\lambda_N = 0.06\text{V}^{-1}$, and $\lambda_P = 0.08\text{V}^{-1}$, design a folded cascode comparator that meets the following specifications. Assume

$V_{DD} = 2.5\text{V}$	$t_p = 10\mu\text{s}$	$V_{OH} = 2.25\text{V}$	$V_{OL} = 0.25\text{V}$	$V_{in}(\text{min}) = 1\text{mV}$	$1\text{V} \leq \text{ICMR} \leq 2\text{V}$
------------------------	-----------------------	-------------------------	-------------------------	-----------------------------------	---

- $A_v(0) = (V_{OH} - V_{OL}) / V_{in}(\text{min}) = 1.75\text{V} / 1\text{mV} = 1750\text{V}/\text{V}$
- $g_{m1} = \frac{0.693 A_v(0)}{t_p} C_L = \frac{0.693 \times 1750 \times 10\text{pF}}{10\mu\text{s}} = 1.213\text{mS}$
- Choose $I_3 = 100\mu\text{A}$. $\frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{g_{m1}^2}{2K_N' I_3} = \frac{(1.218 \times 10^{-3})^2}{2 \times 120 \times 10^{-6} \times 100 \times 10^{-6}} = 61.3$
- $V_{GS1} = \sqrt{I_3 / K_N' \left(\frac{W_1}{L_1} \right)} + V_{T1} = 0.616\text{V} \Rightarrow$
 $\frac{W_3}{L_3} = \frac{2I_3}{K_N' (\text{ICMR} - V_{GS1})^2} = \frac{200}{120(1 - 0.61)^2} = 11.3$
- Choose $I_4 = I_5 = 125\mu\text{A}$. $W_4/L_4 = W_5/L_5 = 4I_4 / [K_P' (V_{DD} - V_{OH})^2] = 500 / [25(0.25)^2] = 320$
- $W_6/L_6 = W_7/L_7 = 4I_6 / [K_P' (V_{DD} - V_{OH})^2] = 300 / [25(0.25)^2] = 192$
- $\frac{W_8}{L_8} = \frac{W_9}{L_9} = \frac{W_{10}}{L_{10}} = \frac{W_{11}}{L_{11}} = \frac{4I_6}{K_N' V_{OL}^2} = 300 / [120(0.25)^2] = 40$

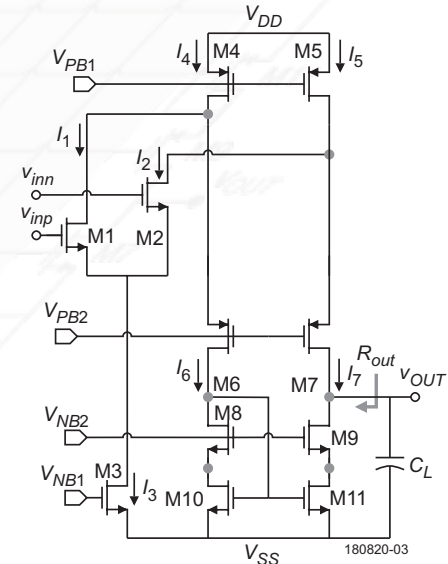

Two-Stage Comparators

Propagation delay time:

The step response of a comparator with two real axis poles ($p_1 \neq p_2$) is,

$$v_{out}(t) = A_V(0)V_{in} \left[1 + \frac{p_2 e^{-t|p_1|}}{p_1 - p_2} - \frac{p_1 e^{-t|p_2|}}{p_1 - p_2} \right]$$

Normalizing in amplitude and time gives,

$$v'_{out}(t_n) = \frac{v_{out}(t)}{A_v(0)V_{in}} = 1 + \frac{m}{1-m} e^{-t_n} - \frac{1}{1-m} e^{-mt_n}$$


where $m = p_2/p_1 \neq 1$ and $t_n = t|p_1|$

If $p_1 = p_2$, then the normalized output voltage is,

$$v'_{out}(t) = 1 - e^{-t|p_1|} - t|p_1|e^{-t|p_1|}$$

$$v'_{out}(t_n) = 1 - e^{-t_n} - t_n e^{-t_n}$$

A graph of the output is shown.

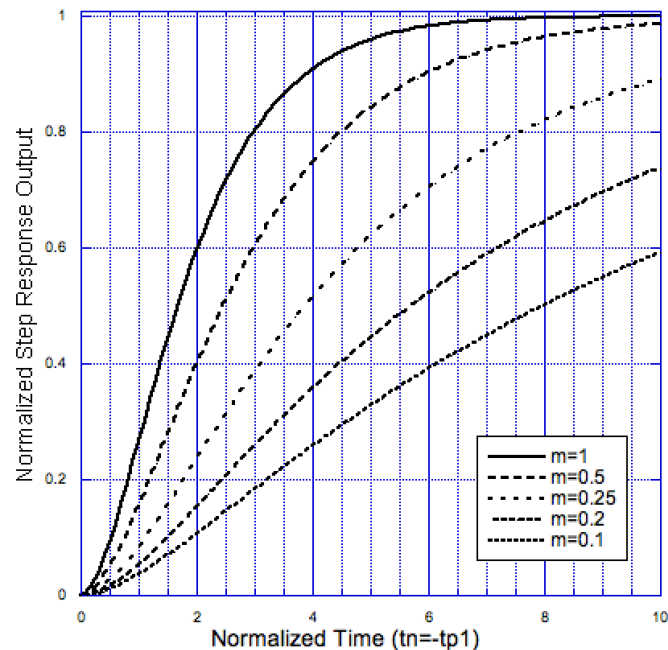

Two-Stage Comparators

Propagation delay time - Continued:

To find the propagation delay time, t_p , equate amplitude unnormalized output to $0.5(V_{OH}-V_{OL})$.

$$v_{out}(t_{pn}) = A_v(0)V_{in} \left[1 - \frac{m}{m-1} e^{-t_{pn}} + \frac{1}{m-1} e^{-mt_{pn}} \right] = 0.5(V_{OH} - V_{OL})$$

Approximating the exponential terms with a power series and taking the dominant terms, the propagation time delay can be expressed as,

$$t_{pn} \approx \sqrt{\frac{V_{OH}-V_{OL}}{mA_v(0)V_{in}}} = \sqrt{\frac{V_{in}(\min)}{mV_{in}}} = \frac{1}{\sqrt{mk}} \Rightarrow t_p = \frac{1}{|p_1|\sqrt{mk}} = \frac{1}{\sqrt{k p_1 p_2}}$$

If we assume $k=1$ where $V_{in} = V_{in}(\min)$, then

$$|p_1| = \frac{1}{|p_2|t_p^2} \quad \text{and} \quad |p_1| = \frac{1}{R_1 C_1} = \frac{(\lambda_n + \lambda_p)I_5}{2C_1} \quad \text{also} \quad |p_2| = \frac{1}{R_2 C_L} = \frac{(\lambda_n + \lambda_p)I_7}{C_L}$$


where C_1 is the capacitance to ground at the output of the first stage. Equating the two expressions for $|p_1|$, substituting for $|p_2|$, and solving for C_1 gives,

$$C_1 = \frac{(\lambda_n + \lambda_p)^2 I_5 I_7 t_p^2}{2C_L}$$

Two-Stage Comparator Design

Design Procedure – C03:

Step	Design Equations	Comments
This design procedure assumes $V_{in} = V_{in}(\min)$ or $k = 1$		
1	$A_v(0) = (V_{OH} - V_{OL}) / V_{in}(\min)$	V_{OH} , V_{OL} , $V_{in}(\min)$ given
2	$C_1 = \frac{(\lambda_n + \lambda_p)^2 I_5 I_7 t_p^2}{2C_L}$	Choose I_5 and I_7 . t_p and C_L are assumed to be given.
3	$\frac{W_6}{L_6} = \frac{2I_7}{K'_p(V_{DD} - V_{OH})^2}$ and $\frac{W_7}{L_7} = \frac{2I_7}{K'_n(V_{OL} - V_{SS})^2}$	$V_{DD} - V_{OH} = V_{sd6}(\text{sat})$ and $V_{OL} = V_{ds7}(\text{sat})$
4	$\frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{A_v^2(0) I_5 I_7 (\lambda_n + \lambda_p)^2}{4K'_n K'_p (W_6/L_6)}$	$g_{m1} = \frac{A_v(0)}{g_{m6} R_1 R_2}$ $g_{m1} = \sqrt{I_5 K'_n (W_1/L_1)}$
5	$\frac{W_5}{L_5} = \frac{I_5}{I_7} \frac{W_7}{L_7}$ or $\frac{W_5}{L_5} = \frac{2I_5}{K'_n (ICMR^- - V_{GS1})^2}$, $ICMR^- > V_{GS1}$	W_5/L_5 should satisfy both relationships if possible
6	$\frac{W_3}{L_3} = \frac{W_4}{L_4} = \frac{I_5}{K'_3 [V_{DD} - ICMR^+ - V_{T3} + V_{T1}]^2}$	$ICMR^+ = V_{in}(\max)$ specified, $M3 = M4$

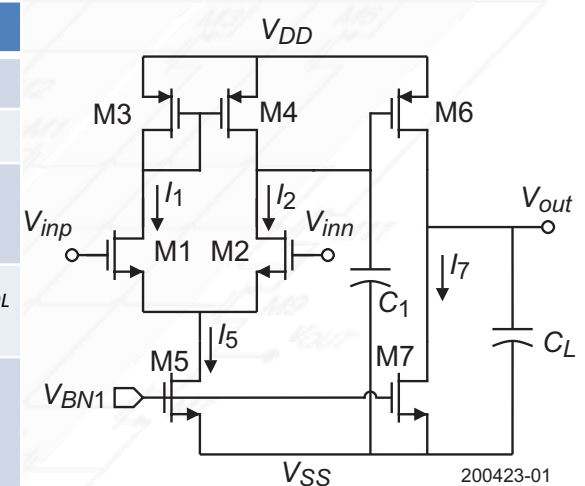

Example 3

$$1. A_V(0) = (V_{OH} - V_{OL}) / V_{in(min)} = 2V / 1mV = 2000V/V$$

2. Choose $I_5=10\mu\text{A}$ and $I_7=50\mu\text{A}$

$$C_1 = \frac{(\lambda_n + \lambda_p)^2 I_5 I_7 t_p^2}{2C_L} = \frac{(0.06 + 0.08)^2 10\mu A \times 50\mu A \times 1\mu s^2}{2 \times 10pF} = 0.49pF$$

$$3. \frac{W_6}{L_6} = \frac{2I_7}{K'_n(V_{DD}-V_{OH})^2} = \frac{2 \times 50 \mu A}{25 \times 10^{-6} \times 0.25^2} = 64 \text{ and } \frac{W_7}{L_7} = \frac{2I_7}{K'_n(V_{OL}-V_{SS})^2} = \frac{2 \times 50 \mu A}{120 \times 10^{-6} \times 0.25^2} = 13.33$$


$$4. \frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{A_v^2(0)I_5I_7(\lambda_n + \lambda_p)^2}{4K_n'K_p'(W_6/L_6)} = \frac{2000^2 \times 10\mu A \times 50\mu A \times (0.06 + 0.08)^2}{4 \times 120 \times 10^{-6} \times 25 \times 10^2 \times 64} = 51.04$$

$$5. \frac{W_5}{L_5} = \frac{I_5}{I_7} \frac{W_7}{L_7} = \frac{10}{50} \times 13.33 = 2.67 \text{ or } \frac{W_5}{L_5} = \frac{I_5}{K'_N (ICMR - V_{GS1})^2} = \frac{20}{120(1-0.54)^2} = 0.78$$

$$V_{GS1} = \sqrt{I_5/K'_N \left(\frac{W_1}{L_1}\right)} + V_{T1} = 0.54V$$

$$6. \frac{W_3}{L_3} = \frac{W_4}{L_4} = \frac{I_5}{K'_{I3}[V_{DD}-ICMR^+ - |V_{T3}| + V_{T1}]^2} = \frac{10}{25 \times (2.5-2)^2} = 1.6$$

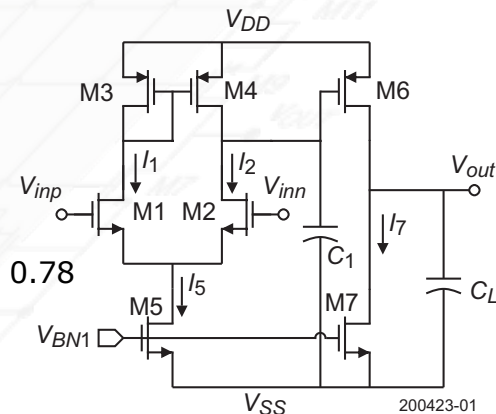It turns out that $C_{GS6} = 52.5\text{fF}$ so C_1 should be changed to 0.438pF . Also, $m = [I_5 / (2xI_7)](C_1/C_l) = 0.49$.



Open Loop Comparator Design

Summary:

- Types of op amps
- Simple one-stage comparator
 - Design procedure CO1
 - Example 1
- Folded cascode comparator
 - Design procedure CO2
 - Example 2
- Two-stage comparator
 - Design procedure CO3
 - Example 3

Change Tracking

Date	Slide No.	Correction or change
11/11/19	7	Steps 1 and 8 have been changed to include the influence of I_{10}
11/11/19	9	Step 7 has been modified to include I_{10}
6/12/20	6	Added to the second bullet – “so that the current becomes constant.”
6/12/20	9	Added under comments on line 8 “Can change currents if too large.”